

## Homework #9

Dr. Ramy Gohary

1. Second-order response: In the RLC circuit shown in Figure 1, let  $E = 1$  volt,  $L = 1$  Henry and  $C = 0.5$  Farad. The switch was open for a long time and was closed at  $t = 0$ . Assume zero initial conditions.

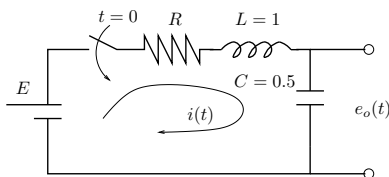


Figure 1: Second order electrical system

- Derive an expression for the Laplace transform of the voltage across the capacitor for arbitrary  $R$ .
  - Is the system underdamped or overdamped with  $R = 1$  Ohm?
  - What is the steady-state value of  $e_o(t)$ ? Sketch  $e_o(t)$  versus  $t$ .
  - What is the natural frequency of the system,  $\omega_n$ ? What is the damping ratio,  $\zeta$ ?
  - What is the value of  $R$  for which the system is critically damped?
2. Consider the system in Figure 2. Assume zero initial conditions and let  $b = 4$  Nt.s/m and  $m = 1$  Kg.
- Obtain the differential equation that describes the displacement  $y$  when the input force is  $p(t) = u(t)$  and  $k$  is arbitrary.
  - Suppose that  $k = 2$ . Is the system underdamped, critically damped or over damped?
  - What is the natural frequency of the system,  $\omega_n$ ? What is the damping ratio,  $\zeta$ ?
  - What is the value of  $k$  for which the system is critically damped?

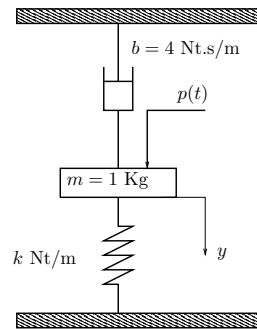


Figure 2: Second order mechanical system