
SYSC3601

Microprocessor Systems

Unit 5:

Memory Structures and Interfacing

Topics/Reading

1. Memory Types
2. Interfacing 8-bit memory/IO (8088)
3. Interfacing 16-bit memory/IO (8086)
4. Interfacing 32/64-bit memory/IO

Reading: Chapter 10, skim 10-5 &10-6

Memory Types

Read-Only Memory (ROM)

Non-volatile!

ROM Read-Only Memory

programmed during fabrications at factory.

control program in dedicated μ P systems is stored in ROM.

PROM Programmable Read-Only Memory.

programmed by burning (blowing) tiny Nichrome or silicon-oxide fuses.

Once programmed, it cannot be erased.

Memory Types

Read-Only Memory (ROM) con't

EPROM Erasable Programmable Read Only Memory.

Memory can be erased by exposure to UV light (up to 20min)

can be programmed by user, but it is usually removed to be erased.

Ex: 2716, 2764, 27256.

EEPROM Electrically Erasable Programmable Read-Only Memory

Also called Flash Memory™ (Intel), or EARM (Electrically Alterable ROM).

Can be erased and reprogrammed in and by the system.

Memory Types

Random Access Memory (RAM)

2 types:


1) Static (SRAM)

Retains data for as long as power is applied

FAST, EXPENSIVE, BIG

higher gate count – 4 or 6, needs a flip flop

Used for cache

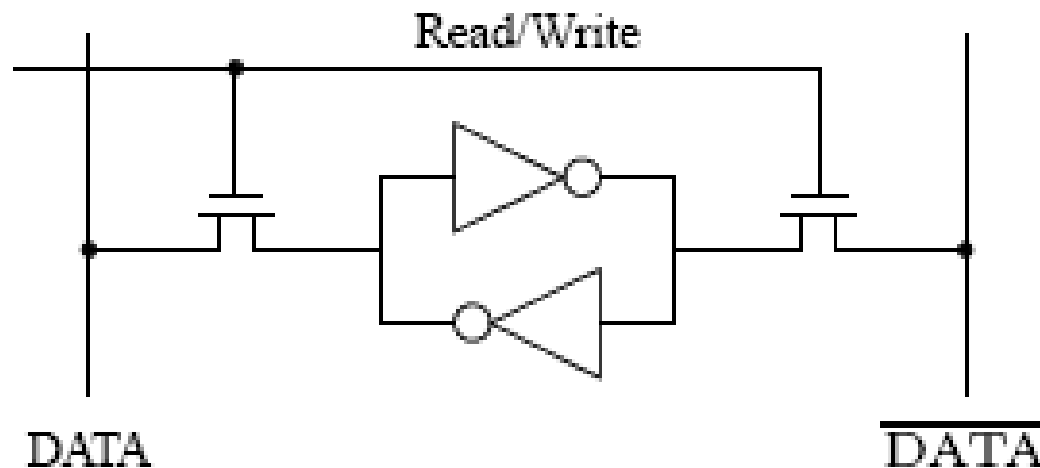

Memory Types

Random Access Memory (RAM) con't


2) Dynamic (DRAM)

Retains data for only 2-4ms, then must be refreshed.

Slower but cheaper and can be larger (e.g. 2GB DIMM)


High density (1 transistor plus capacitor)

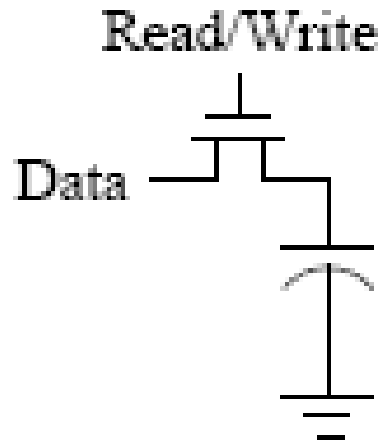Usually use a DRAM controller to handle interfacing and refresh.



Memory Types

DRAM devices

 


- Address pins are *multiplexed!*
- A_0 - A_7 loaded first with \overline{RAS} (row address select).
- A_8 - A_{15} loaded second with \overline{CAS} (column address select).
- \overline{CAS} also serves as chip select.

Figure 1: TMS 4464
DRAM

Memory Types

DRAM Organization

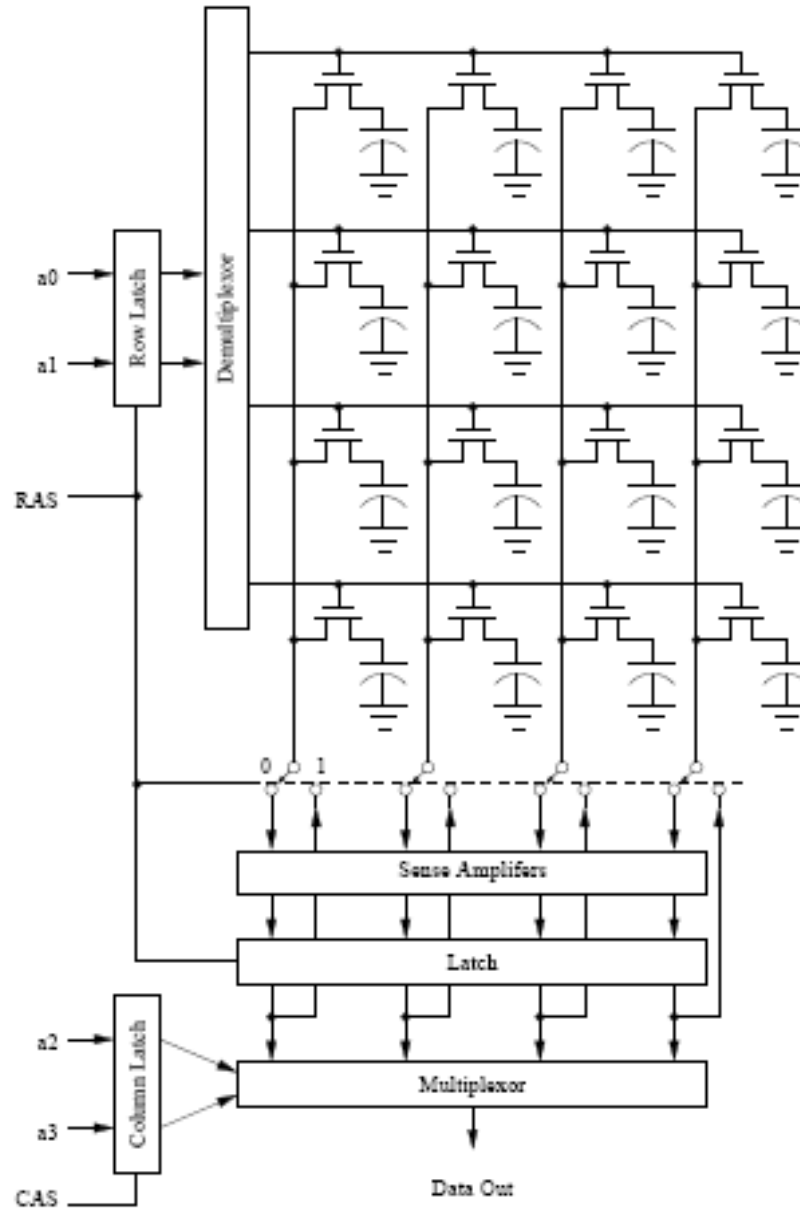

Memory Types

DRAM types

EDO Extended Data output DRAM.

- bits selected by $\overline{\text{RAS}}$ are latched.
- faster for sequential address - no wait states for sequential accesses.

SDRAM Synchronous DRAM


- faster (access times 10nS-8nS).
- internal state machine tied to system clock controlling operation.
- Used for “burst-read ” 4 64-bit numbers.

DDR Double data rate. (sequences at twice system clock)

RDRAM Rambus DRAM.

Memory & I/O Interfacing

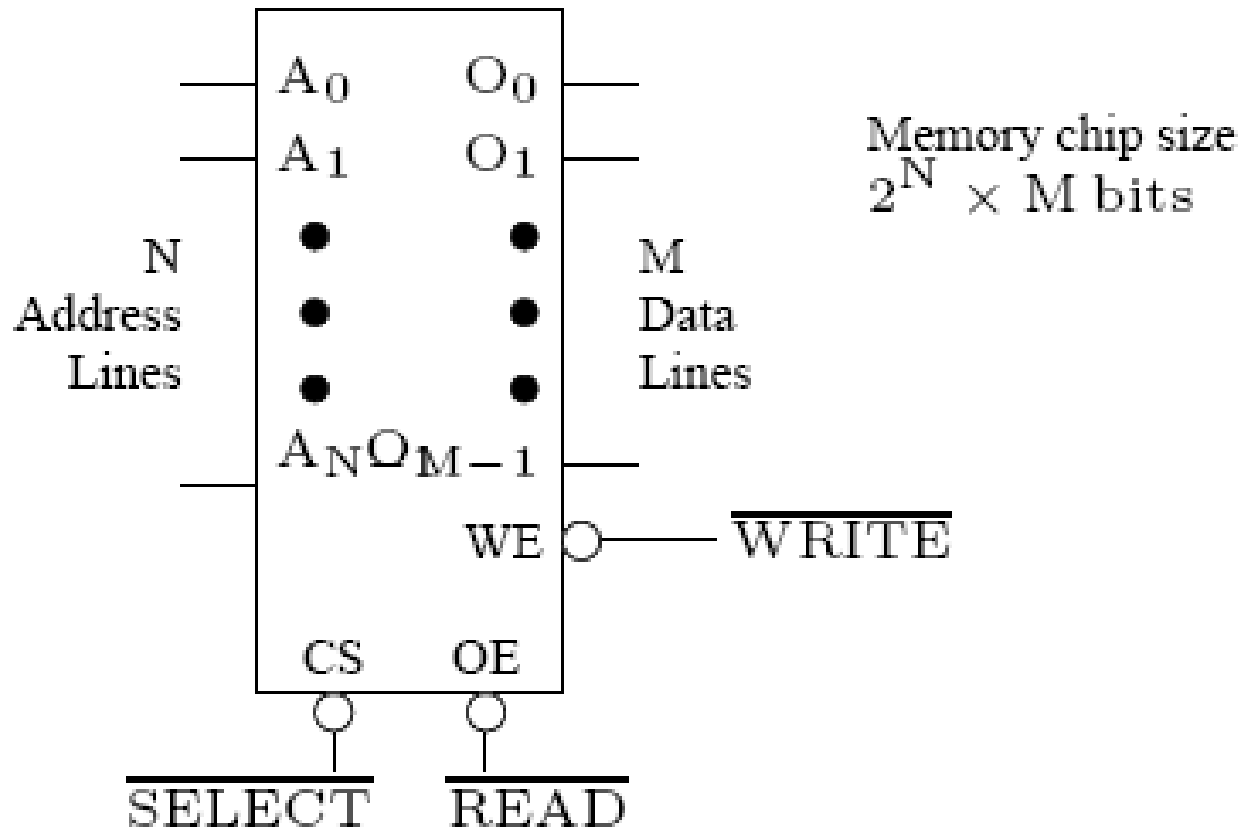General steps for memory and I/O interfacing
Generic memory device:



Memory & I/O Interfacing

N address lines can address 2^N memory locations:

| | Size | | Lines | Range |
|----|----------|----------|-------|--------------|
| 1k | 1024 | 2^{10} | 10 | 00000-003FF |
| 2k | 2048 | 2^{11} | 11 | 00000-007FF |
| 4k | 4096 | 2^{12} | 12 | 00000-00FFF |
| 1M | 10848576 | 2^{20} | 20 | 00000-FFFFFF |

Memory & I/O Interfacing

Steps to success:

1) Architectural questions:

How many chips are required?

How many address lines go to each chip?

How will chips be organized into banks and which parts of the address bus will be used?

2) Determine address range:

Typically problem is to place devices within memory map

Determine START, SIZE, LO (=START), HI (=LO+SIZE-1)

Determine CONST, SEL, and MEM address lines

3) Generate overall chip select signal (MSEL) from CONST portion of address range and M/I/O

4) Generate bank-specific write signals if required

5) Complete interface design! (often using decoders)

Be sure to connect address bus, data bus, and control bus (RD, WR)

Memory & I/O Interfacing Example 1


Ex: Design an interface for an 8088 μ P to connect a single 2716 (2K x 8) EPROM such that memory starts at address FF800H.

Notes:

The 8088 has 20 address lines and 8 data lines (assuming that it is already fully demultiplexed and buffered)

The 2716 has 1 \overline{CS} (chip select) pin and one \overline{OE} (output enable) pin.

 Standard logic gates (NAND, NOR, NOT) may be used.



Memory & I/O Interfacing Example 1

Steps to success:

1) Architectural questions:

How many chips are required? **ONE**

How many address lines go to each chip?

The 2716 has $2k = 21 \times 210 = 211$ locations, so we need 11 address lines to the 2716 chip.

How will chips be organized into banks and which parts of the address bus will be used?

Only 8-bit data bus -> only one bank. No bank-enable signals required.

2) Determine address range:

START =

SIZE =

LO (=START) =

HI (=LO+SIZE-1)

Determine CONST, SEL, and MEM address lines

3) Generate overall chip select signal from CONST portion of address range and M/IO

4) Generate bank-specific write signals if required

5) Complete interface design! (often using decoders)

Be sure to connect address bus, data bus, and control bus (RD, WR) — —

Memory & I/O Interfacing Example 1

Steps to success:

- 1) Architectural questions:
- 2) Determine address range:

START = FF800h

SIZE = 800h (2K)

LO (=START) = FF800h

HI (=LO+SIZE-1) = FFFFFh (FF800h+800h-1)

Determine CONST, SEL, and MEM address lines:

| | | | | | | | | | | | | | | | | | | | |
|----------------|----|----|----|----|----|----|----|----|------------------|---|---|---|---|---|---|---|---|---|---|
| 19 | 18 | 17 | 16 | 15 | 14 | 13 | 12 | 11 | 10 | 9 | 8 | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| CONST (decode) | | | | | | | | | To Memory Device | | | | | | | | | | |


Memory & I/O Interfacing Example 1

Steps to success:

1) Architectural questions:

2) Determine address range:

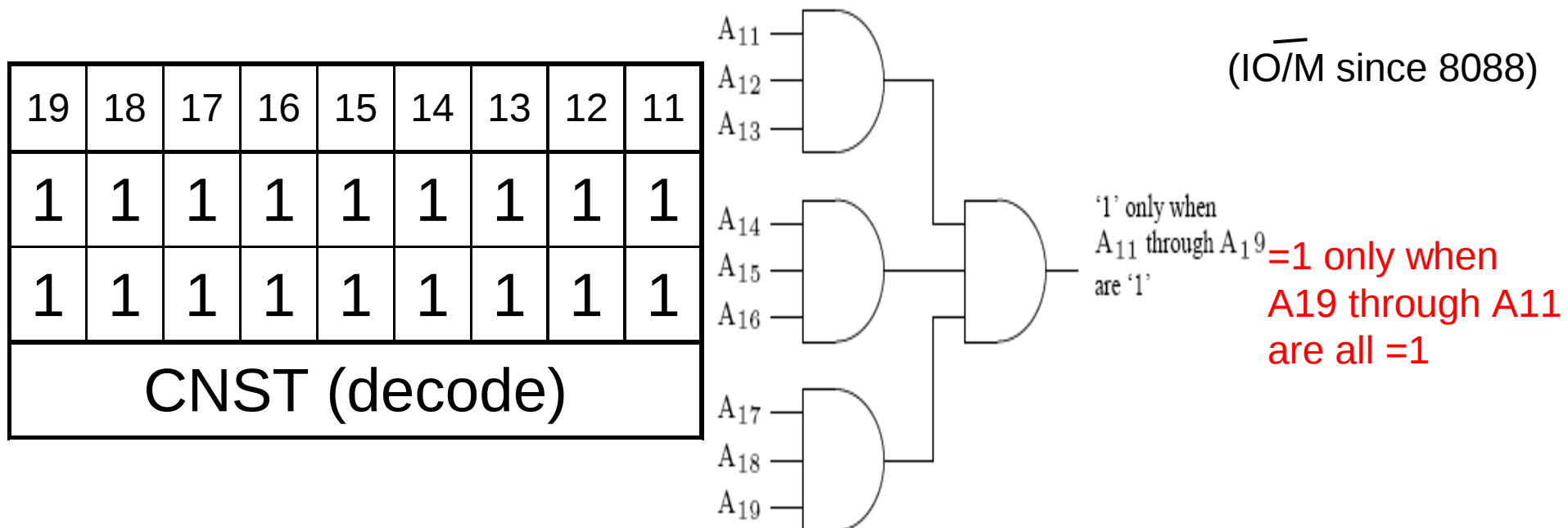3) Generate overall chip select signal from CONST portion of address range and M/I/O:




8-bit Memory Interfacing Example 1

- 4) Generate bank-specific write signals if required **NOT**
- 5) Complete interface design! (often using decoders)

Be sure to connect address bus, data bus, and control bus (RD, WR):

From previous slide...

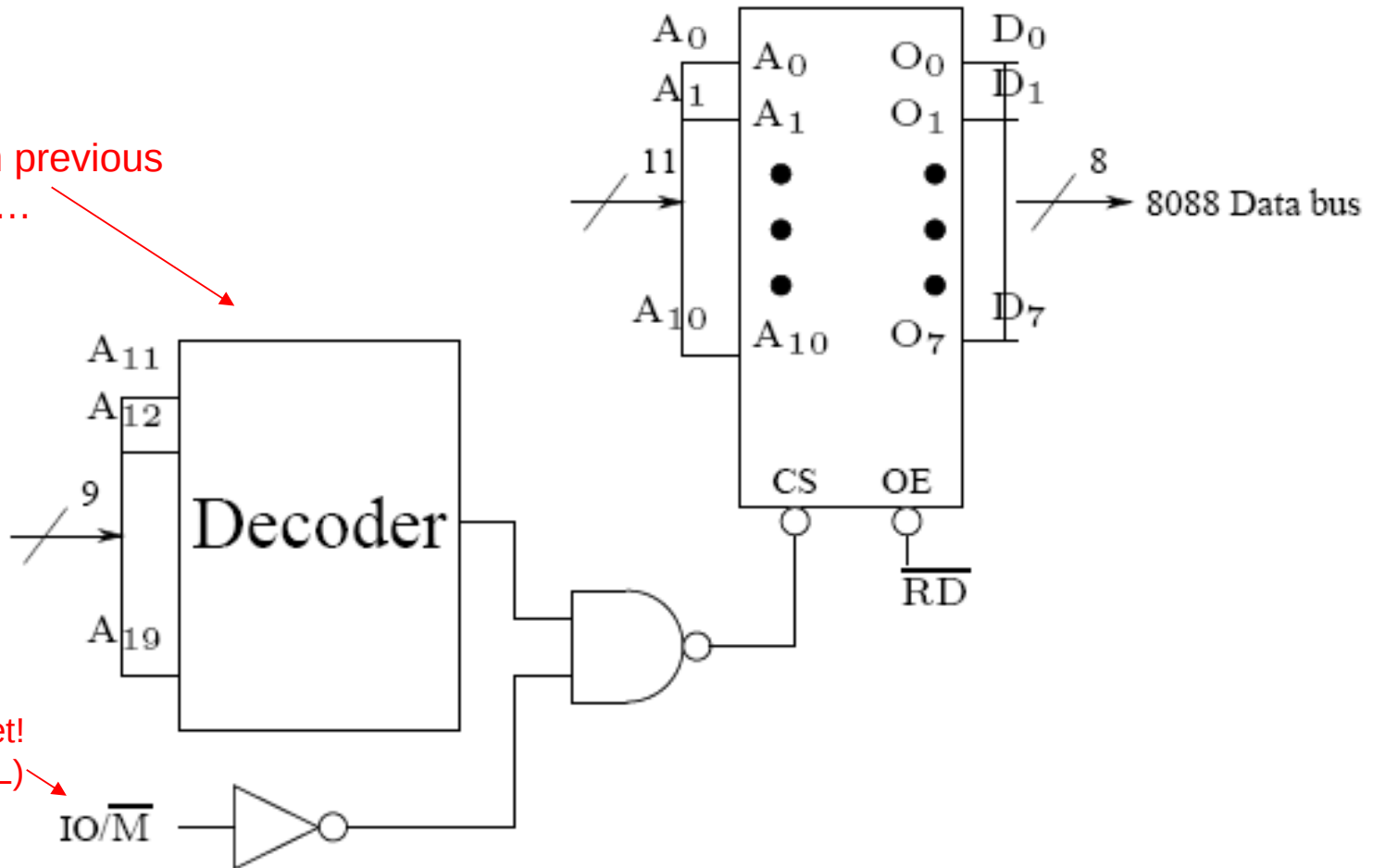

Don't forget!
(can include in SEL)

Address Decoding

Notes on Address Decoding


Address range will look something like this:

| | | | | | | | | | | | | | | | | | | | |
|-----------------|----|----|----|----|----|----|----|------------|----|---|----------------------|---|---|---|---|---|---|---|---|
| 19 | 18 | 17 | 16 | 15 | 14 | 13 | 12 | 11 | 10 | 9 | 8 | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | D | D | D | M | M | M | M | M | M | M | M | M |
| Constant | | | | | | | | Sel | | | Memory device | | | | | | | | |

- 1) **Constant**: to decoder or gate logic to select bank or enable decoders for DDD.
- 2) **DDD**: to decoder to select a memory device.
- 3) **MMM**: to memory devices depending on available address pins.

Address Decoding

Logic decoders:

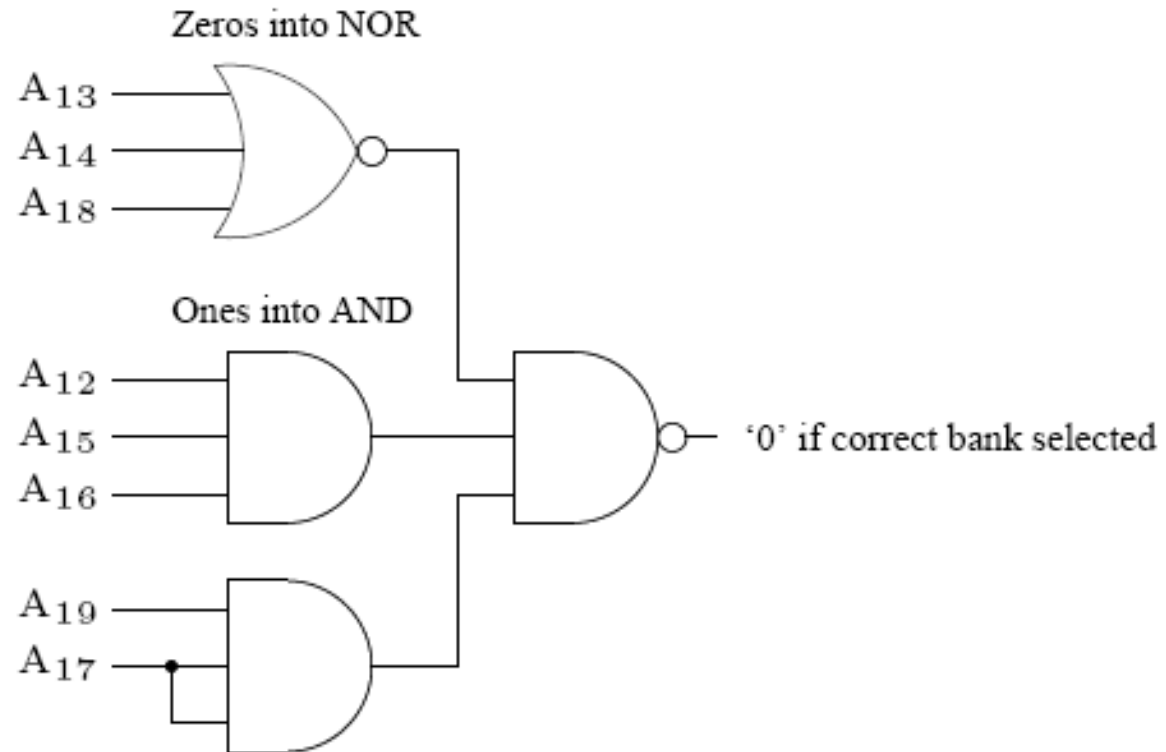

1. Must also decode $\overline{IO/\overline{M}}$.
2. Must use \overline{RD} or \overline{WR}

Address Decoding

Programmable Decoders

PLD Programmable logic device

Arrays of logic elements that are programmable.

3 types:

PLA Programmable logic array

PAL Programmable array logic

GAL Gated array logic

PAL has replaced PROM address decoders in latest memory interfaces.


typically constructed with AND/OR/NOT logic.

PALs are programmed using software such as PALASM.

Many examples in text use PAL decoders.

In class, we will use logic gates directly, but in practice, PALs can reduce the chip count.

Sample PLD

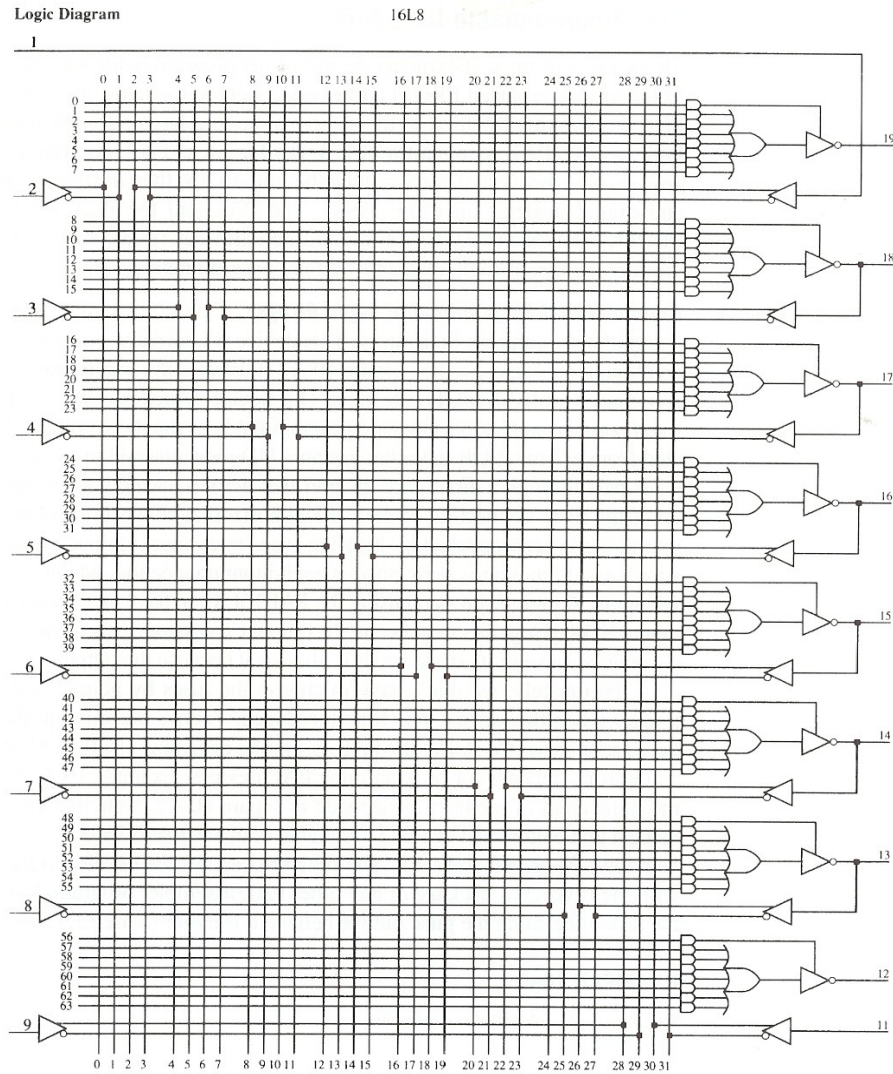


Address Decoding

The 74LS138 3-to-8 decoder

- Y_n goes low whenever:
 1. $G1='1'$ and $G2A = G2B = '0'$.
 2. $n = C \times 4 + B \times 2 + A \times 1$

| | C | B | A | n |
|-----|---|---|---|-----|
| ex: | 0 | 0 | 1 | 1 |
| | 1 | 0 | 1 | 5 |

- Typical time delay is 12nS.

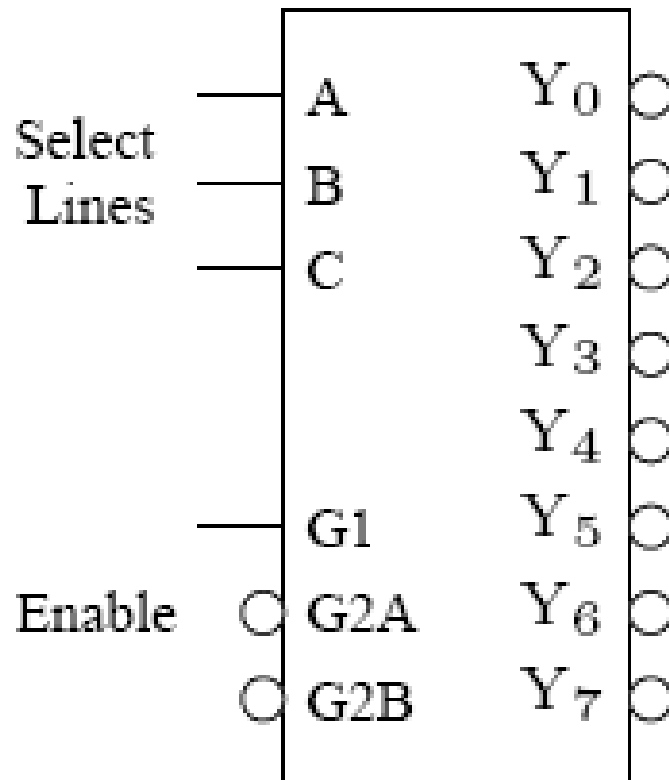

8-bit Memory Interfacing Example 2

Ex: Design a 64k x 8 section of memory for the 8088 using 8k x 8 (2764) EPROMs. The memory start address is A0000H.

Steps to success:

1) Architectural questions:

How many chips are required? **EIGHT**

We need 8 2764s (8k each) for 64k total memory.

How many address lines go to each chip?

The 2764 has $8k = 2^3 \times 2^{10} = 2^{13}$ locations, so we need 13 address lines to each 2764 chip (the same 13 lines go to ALL chips).

How will chips be organized into banks and which parts of the address bus will be used?

Only 8-bit data bus -> only one bank. No bank-enable signals required.

Memory & I/O Interfacing Example 2

Steps to success:

- 1) Architectural questions:
- 2) Determine address range:

We need a $64k = 26 \times 210 = 216$ byte memory block.

START = A0000h

SIZE = 10000h (64K = size of ALL chips put together)

LO (=START) = A0000h

HI (=LO+SIZE-1) = AFFFFh (A0000h+10000h-1)

Determine CONST, SEL, and MEM address lines:

| 19 | 18 | 17 | 16 | 15 | 14 | 13 | 12 | 11 | 10 | 9 | 8 | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
|------|----|----|----|-----|----|----|----|---------------|----|---|---|---|---|---|---|---|---|---|---|
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| CNST | | | | SEL | | | | Memory Device | | | | | | | | | | | |

Will enable decoder


Goes to 74LS138 decoder

Goes to each mem chip

8-bit Memory Interfacing Example 2

- Steps to success:
 - 1) Architectural questions:
 - 2) Determine address range:
 - 3) Generate overall chip select signal from CONST portion of address range and M/IO:


| 19 | 18 | 17 | 16 |
|-------|----|----|----|
| 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| CONST | | | |

 

8-bit Memory Interfacing Example 2

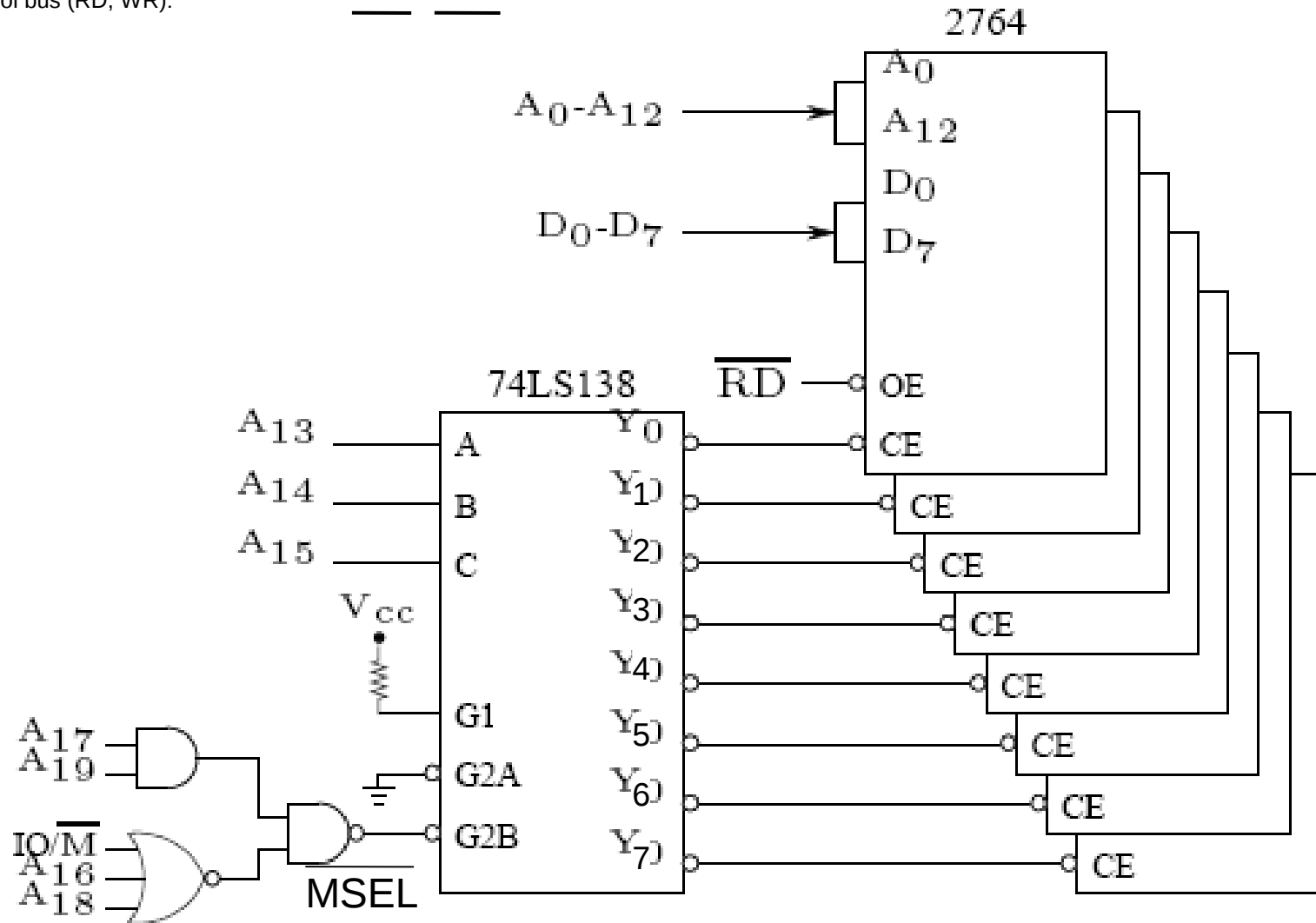- 4) Generate bank-specific write signals if required **NOT REQUIRED**
- 5) Complete interface design! (often using decoders)

Be sure to connect address bus,
data bus, and control bus (RD, WR):



EPRM location in 8088/8086 systems

Note: Normally, the 8088 has EPROM located from F8000H to FFFFFH (upper 32k) since a hardware reset starts execution at FFFF0H.

Note: Slower versions of many 2764 EPROMs have memory access times of 450nS.

8088 allows 460nS.

Decoder ('138) delay is 12nS

Must use READY signal to insert wait state using 8284A clock generator. (*how many?*)


8086 Memory Interface

The 8086 has a 16-bit data bus.

Memory is arranged in two 8-bit banks

low bank: contains all even addresses.

high bank: contains all odd addresses.

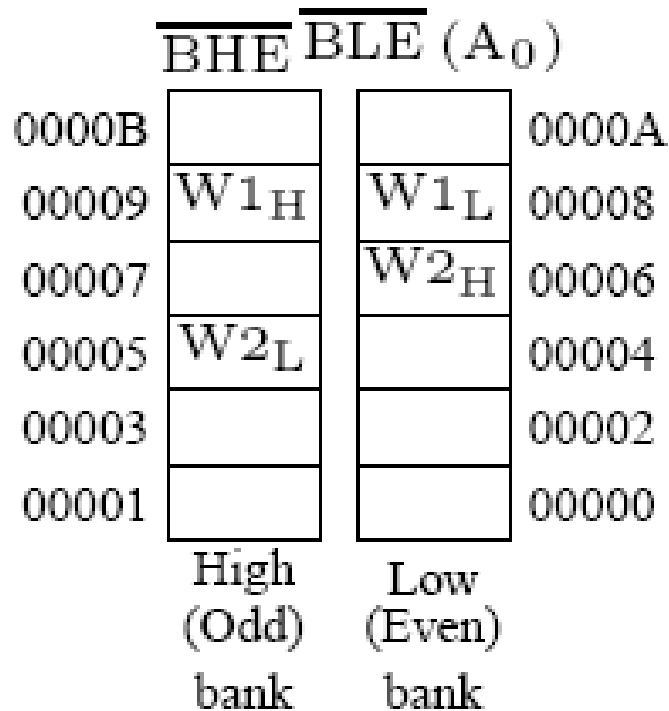

8086 Memory Interface

Aligned/unaligned words

W1 is stored on an even (aligned) address.

It can be accessed in a single read cycle.

W2 is stored at an odd (unaligned) address.

It will require two read cycles (8 T-cycles).

(a) During first read, W2L (odd address) will appear on the high byte of the data bus.

(b) During the second read, W2H (even address) will appear on the low byte of data bus.

During a read operation, both banks may (and often are) activated.

The μ P will read 16-bits for read operations, or will only read the correct half of the data bus for byte operations.

Note that AL may receive data from the high half of the data bus when reading a byte from an odd address!

8086 Memory Interface

Write cycles must activate the correct bank(s) based on BHE and BLE (A0).

BHE is supplied by μP (multiplexed with S7) _____

A0 is used as BLE

i.e. A0=0 for an even address and A0=1 for an odd address

(A0 is not even a pin on the 386 and up)

| $\overline{\text{BHE}}$ | $\overline{\text{BLE}}$ | Function |
|-------------------------|-------------------------|----------------------|
| 0 | 0 | Both banks (16 bits) |
| 0 | 1 | High bank (8 bits) |
| 1 | 0 | Low bank (8 bits) |
| 1 | 1 | No banks enabled |

Memory & I/O Interfacing

Remember the Steps to Success:

1) Architectural questions:

How many chips are required?

How many address lines go to each chip?

How will chips be organized into banks and which parts of the address bus will be used?

2) Determine address range:

Typically problem is to place devices within memory map

Determine START, SIZE, LO (=START), HI (=LO+SIZE-1)

Determine CONST, SEL, and MEM address lines

3) Generate overall chip select signal (MSEL) from CONST portion of address range and M/I/O

4) Generate bank-specific write signals if required

5) Complete interface design! (often using decoders)

Be sure to connect address bus, data bus, and control bus (RD, WR)

16-bit Memory Interfacing Example 1

Design a memory interface for the 8086 which will provide 256k bytes of SRAM, organized as 128k x 16bits, starting at address 40000H and using 62256 SRAM chips (32k x 8bit).

Assume that 8086 address, data, status, and control busses are already demultiplexed and buffered.

1. Architectural questions:

We want 128k x 16 bits

i.e. 128k x 16bits → 4 chips for both the high and low banks.

8 chips total

62256 chips are 32k x 8bit; $32k = 25 \times 2^{10} \leftarrow 15$ address lines

We will use a 2-to-4 decoder (74LS139) to select one out of four chips from each bank.

16-bit Memory Interfacing Example 1

2a. Address Range:

Start address is 40000h

SIZE: 256k bytes is $28 \times 2^{10} \rightarrow 40000\text{h}$ bytes

Therefore address range is:

Low = start = 40000h

High = (start+size-1) = (40000h+40000h-1)
= 7FFFFh

16-bit Memory Interfacing Example 1

2b. Address Decoding:


| | | | | | | | | | | | | | | | | | | | |
|----|----|---------------|----|----|----|----|----|----|----|---|---|---|---|---|---|---|---|---|---|
| 19 | 18 | 17 | 16 | 15 | 14 | 13 | 12 | 11 | 10 | 9 | 8 | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| DD | SS | Address Lines | | | | | | | | | | | | | | | | | B |

D Decode with M/\overline{IO} to select memory

S to 2-to-4 decoder.

B to \overline{BLE}

3. MSEL:

 

16-bit Memory Interfacing Example 1


4. Bank-specific write signals:

The 8086 already handles read from high/low/both banks as needed (W bit)


We must select hi/low/both for write control

5. Design memory interface

Be sure to connect

 

16-bit Memory Interfacing Example 1

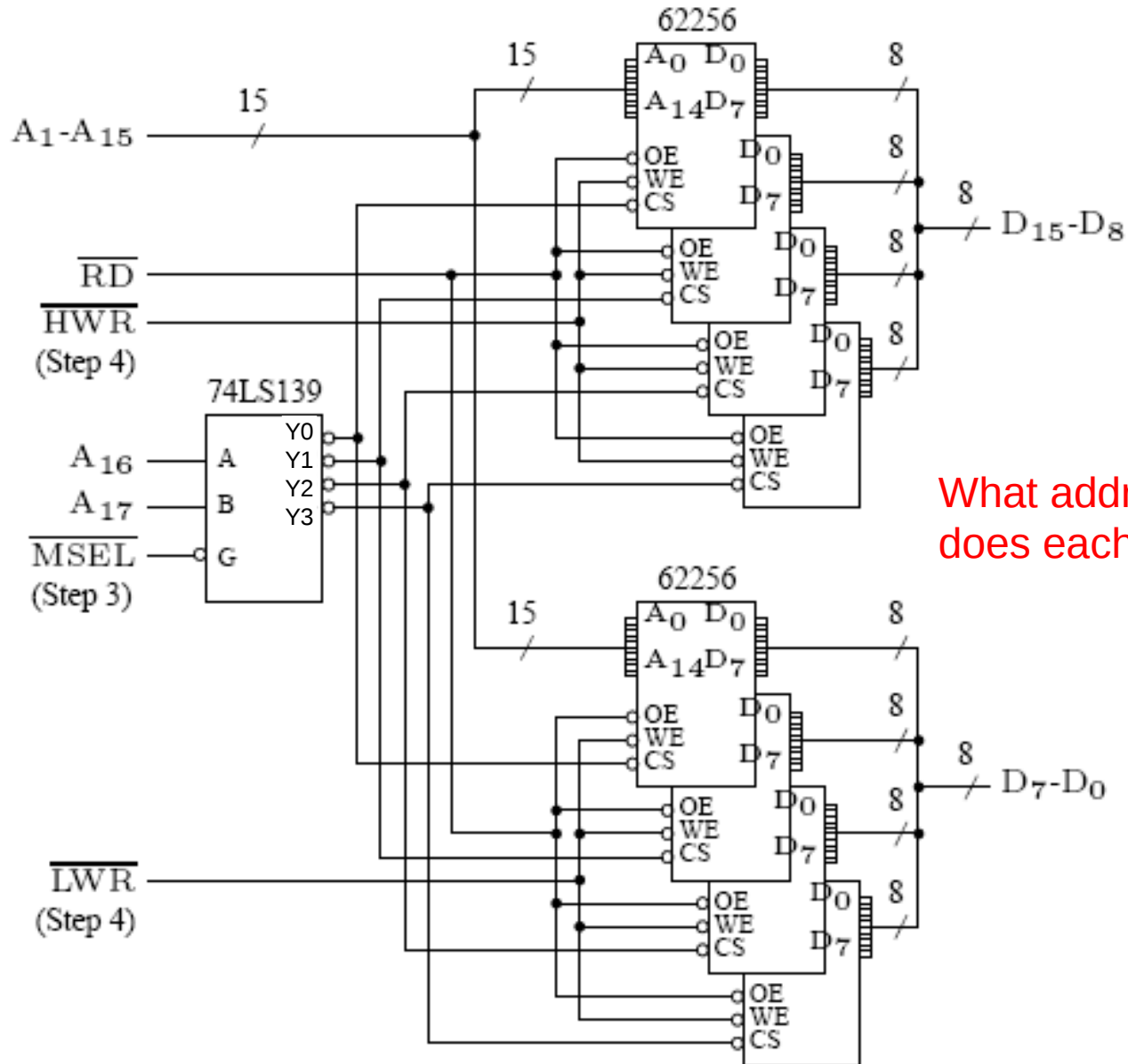


What address range does each chip respond to?

32-bit Wide Memory


Requires 4 banks, each 8-bits wide to generate (up to) 32-bits per read/write

Bank ID is system address 'mod 4'

 Requires 4 bank enable signals for writes:



32-bit Wide Memory

 

64-bit Wide Memory

