

Biopotential Amplifiers

Biopotentials arise from movement of ions in cells and organs. Signal Levels are small + noise levels are large

Electrodes are the biosensor which converts from voltage (as ion potential energy – in tissue)

→

voltage (as electron potential energy – in wires)

Biopotential **amplifiers** are required to

- Amplify signal levels while rejecting interference
- Maintain patient electrical safety

Amplifiers

Slide 03B.2

Amplitude of biomedical signals

Measurement-+	Range	Frequency, Hz	Method
Blood flow	1 to 300 mL/s	0 to 20	Electromagnetic or ultrasonic
Blood pressure	0 to 400 mmHg	0 to 50	Cuff or strain gage
Cardiac output	4 to 25 L/min	0 to 20	Fick, dye dilution
Electrocardiography	0.5 to 4 mV	0.05 to 150	Skin electrodes
Electroencephalography	5 to 300 μ V	0.5 to 150	Scalp electrodes
Electromyography	0.1 to 5 mV	0 to 10000	Needle electrodes
Electroretinography	0 to 900 μ V	0 to 50	Contact lens electrodes
pH	3 to 13 pH units	0 to 1	pH electrode
$p\text{CO}_2$	40 to 100 mmHg	0 to 2	$p\text{CO}_2$ electrode
$p\text{O}_2$	30 to 100 mmHg	0 to 2	$p\text{O}_2$ electrode
Pneumotachography	0 to 600 L/min	0 to 40	Pneumotachometer
Respiratory rate	2 to 50 breaths/min	0.1 to 10	Impedance
Temperature	32 to 40 $^{\circ}$ C	0 to 0.1	Thermistor

Amplifiers

Slide 03B.3

Biopotential Amplifier requirements

Signals are small

Signals are low frequency

- Generally amplifiers should be limited to signal range

Voltage amplifiers required with high input impedance

Electrical shock protection of patient

Common mode (CM voltages are high)

- Active ground required
- High CMRR required

Quick calibration required

Lots of electrical interference in clinical milieu

Adjustable gain (signal levels vary significantly between patients)

Amplifiers

Slide 03B.4



Gain: differential and common mode

In most biomedical measurements, we want to make difference measurements: $v_+ - v_-$

For biopotentials, this is because:

- The signals are inherently differential
- Differential measurements reduce noise

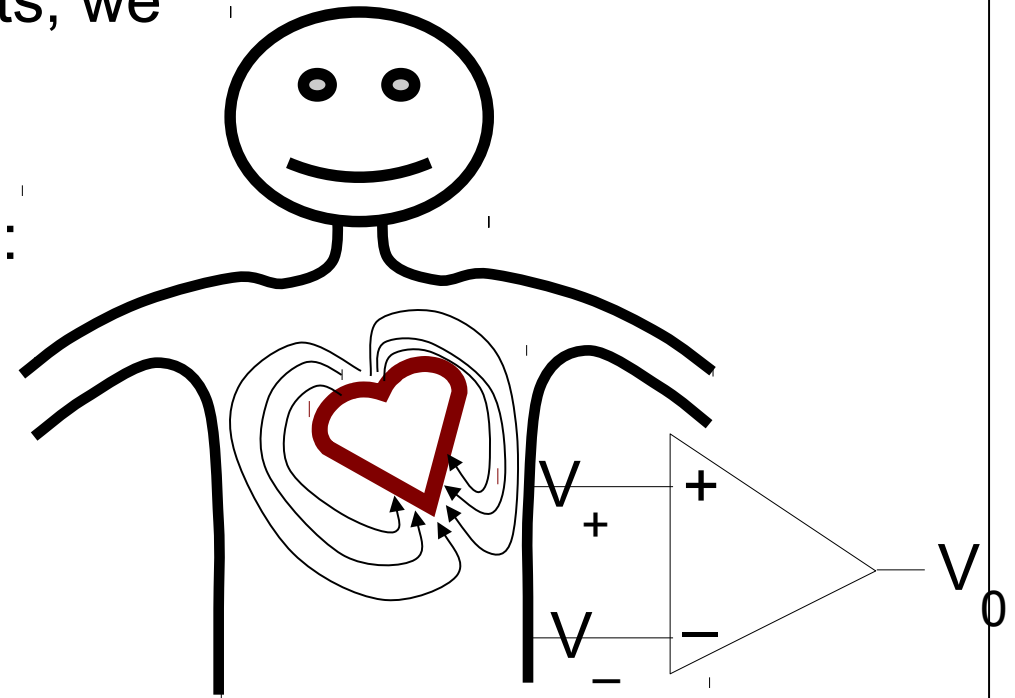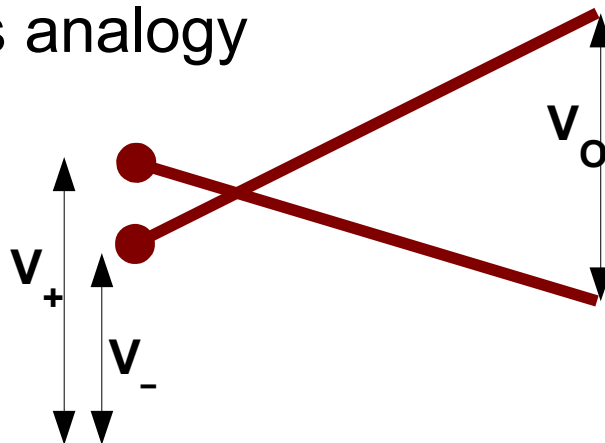Differential gain works using a scissors analogy



Amplifiers

Slide 03B.5

Gain: differential and common mode

Based on difference measurements: $v_+ - v_-$
the output is:

$$V_O = A_d (V_+ - V_-) + A_{cm} V_{cm}$$


where:

$$\text{where } V_{cm} = \frac{V_+ + V_-}{2}$$

- A_d : Differential Gain
- A_{cm} : Common-mode Gain
- $CMRR = A_d / A_{cm}$

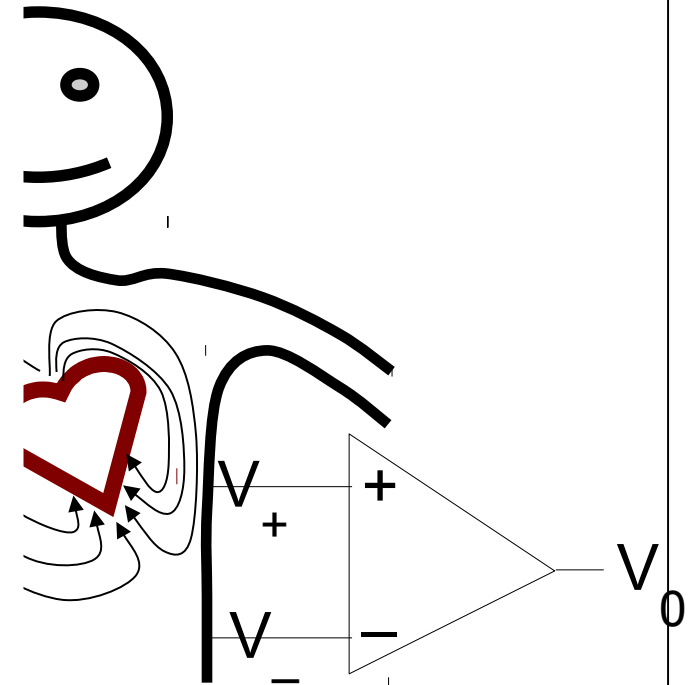Example:

- $V_O = 0.01V$ when $V_- = V_+ = 1V$
- $V_O = 0.02V$ when $V_- = 1V$ & $V_+ = 1V + 1\mu V$
- $A_{cm} = 0.01 \rightarrow A_d = 0.01V / 1\mu V = 10000$
- $CMRR = A_d / A_{cm} = 10^6 \cdot 10000 \rightarrow 20 \log_{10} 10^6 = 120dB$




Amplifiers

Slide 03B.6

Amplifiers: Ideal Op-amp

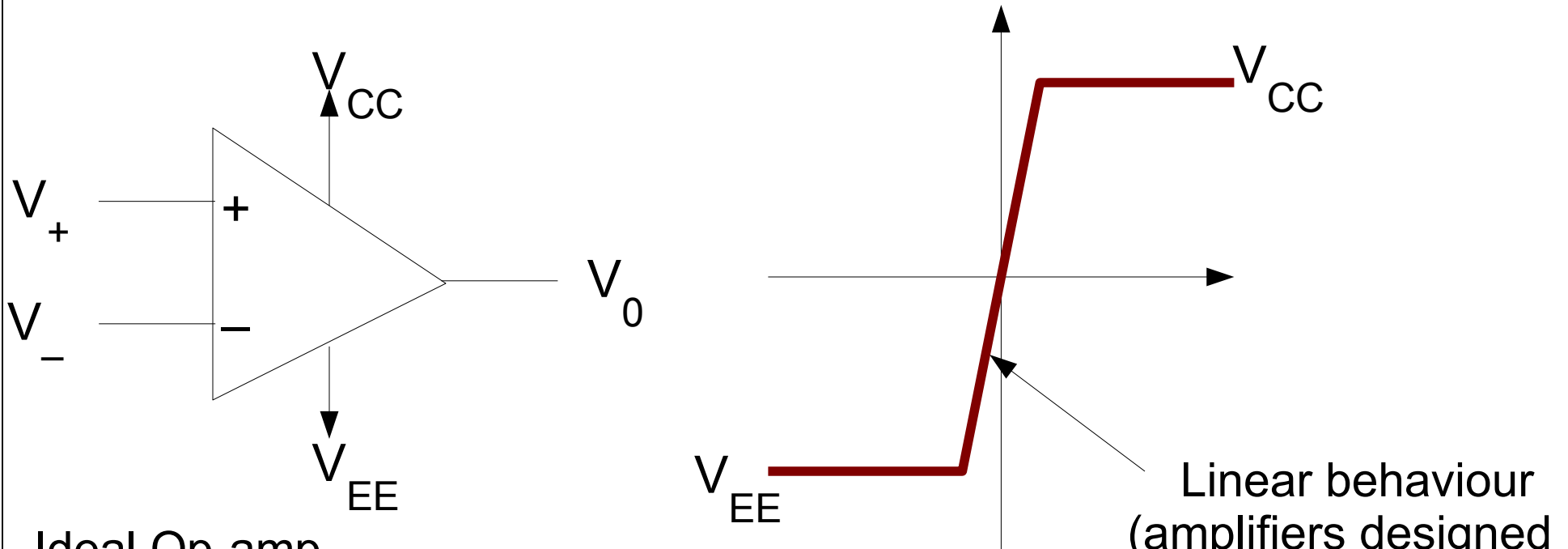The ideal op-amp is the building block for most precision analog circuits



Ideal Op-amp

- Inputs V_+ , V_- draw no current
- Output V_0 can source any current
- When you have negative feedback, V_0 "tries" to make $V_- = V_+$

Linear behaviour
(amplifiers designed
to operate here)

$$V_0 = A(V_+ - V_-)$$

very large $A \approx 100k$

Amplifiers


Slide 03B.7

Amplifier Building Blocks: The difference Amplifier

In most biomedical measurements, we want to make difference measurements ($v_+ - v_-$).

We can use a *difference amplifier*

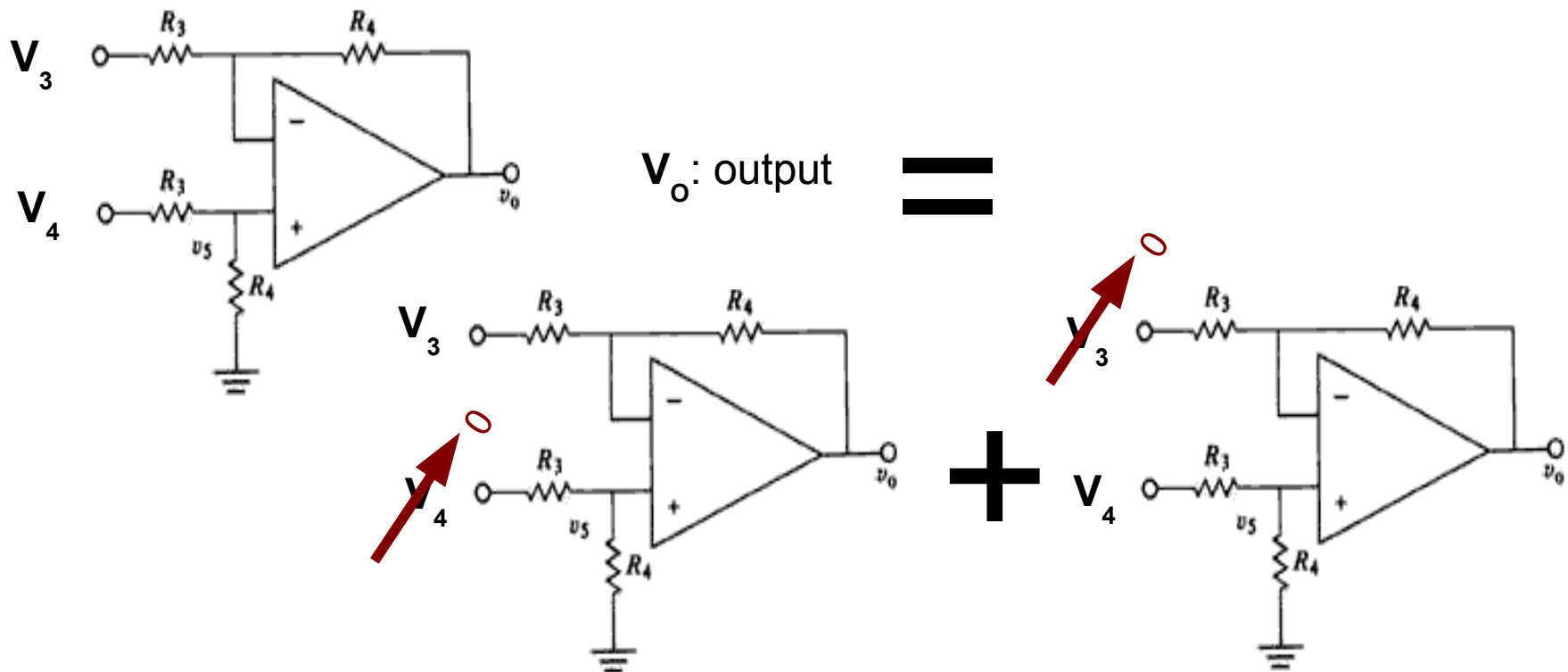
Because the circuits are linear we decompose the difference amp:



Amplifiers

Slide 03B.8

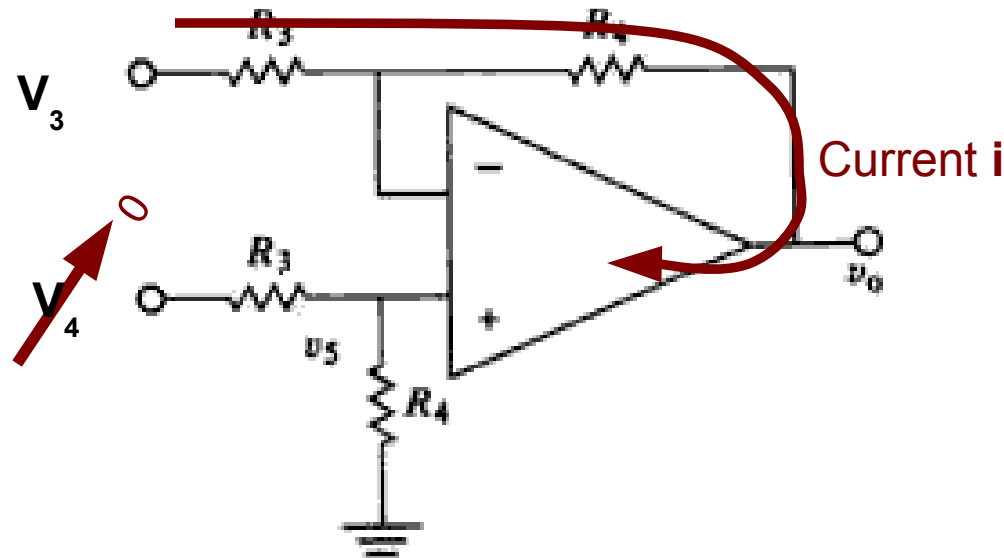Amplifier Building Blocks: the inverting amplifier



Because $V_4 = 0$, $V_+ = 0$

Because V_- draws no current, i flows from V_3 to V_0

We have negative feedback, therefore V_0 does what it can to get $V_- = V_+$.

Since $V_+ = 0$, $V_- = 0$.


Current i : $(V_3 - V_+ = R_3 i) \rightarrow i = V_3/R_3$

Output Voltage: $V_- - V_0 = R_4 i \rightarrow V_0 = -R_4 \frac{V_3}{R_3} = -V_3 \frac{R_4}{R_3}$

Amplifiers

Slide 03B.9

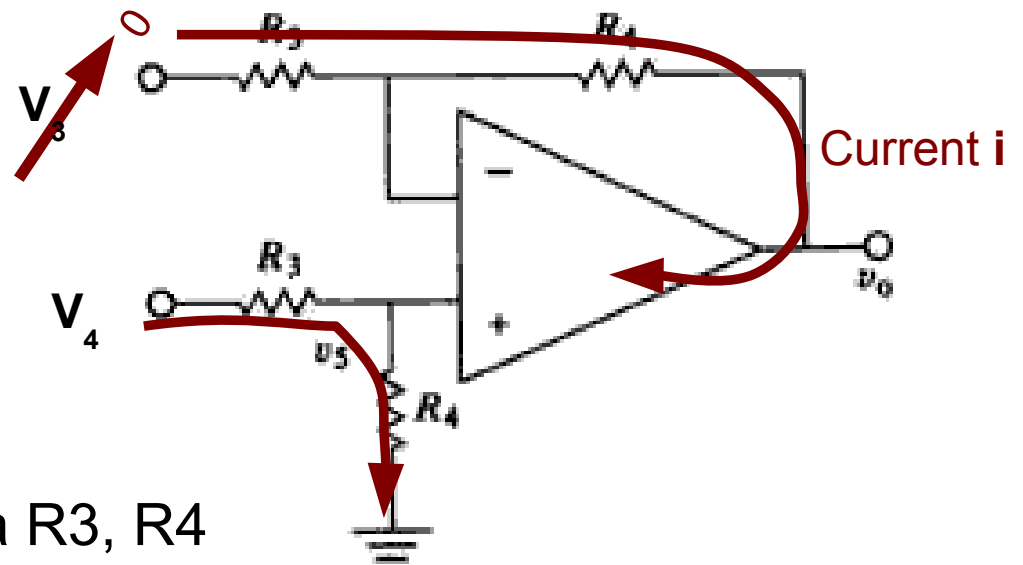Amplifier Building Blocks: the non-inverting amplifier



Current flows from V_4 to ground via R_3 , R_4 acting like a voltage divider.

We have negative feedback, therefore V_o does what it can to get $V_- = V_+$.

Current i :

Output Voltage: $V_- - V_o = R_4 i$

$$V_+ = \frac{R_4}{R_3 + R_4} V_4$$

$$V_3 - V_+ = R_3 i \rightarrow i = \frac{-R_4}{R_3(R_3 + R_4)} V_4$$

$$\frac{R_4}{R_3 + R_4} V_4 - V_o = \frac{-R_4^2}{R_3(R_3 + R_4)} V_4$$


$$V_o = \left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_4}{R_3}\right) V_4 = \frac{R_4}{R_3} V_4$$

Amplifiers

Slide 03B.10

The difference Amplifier

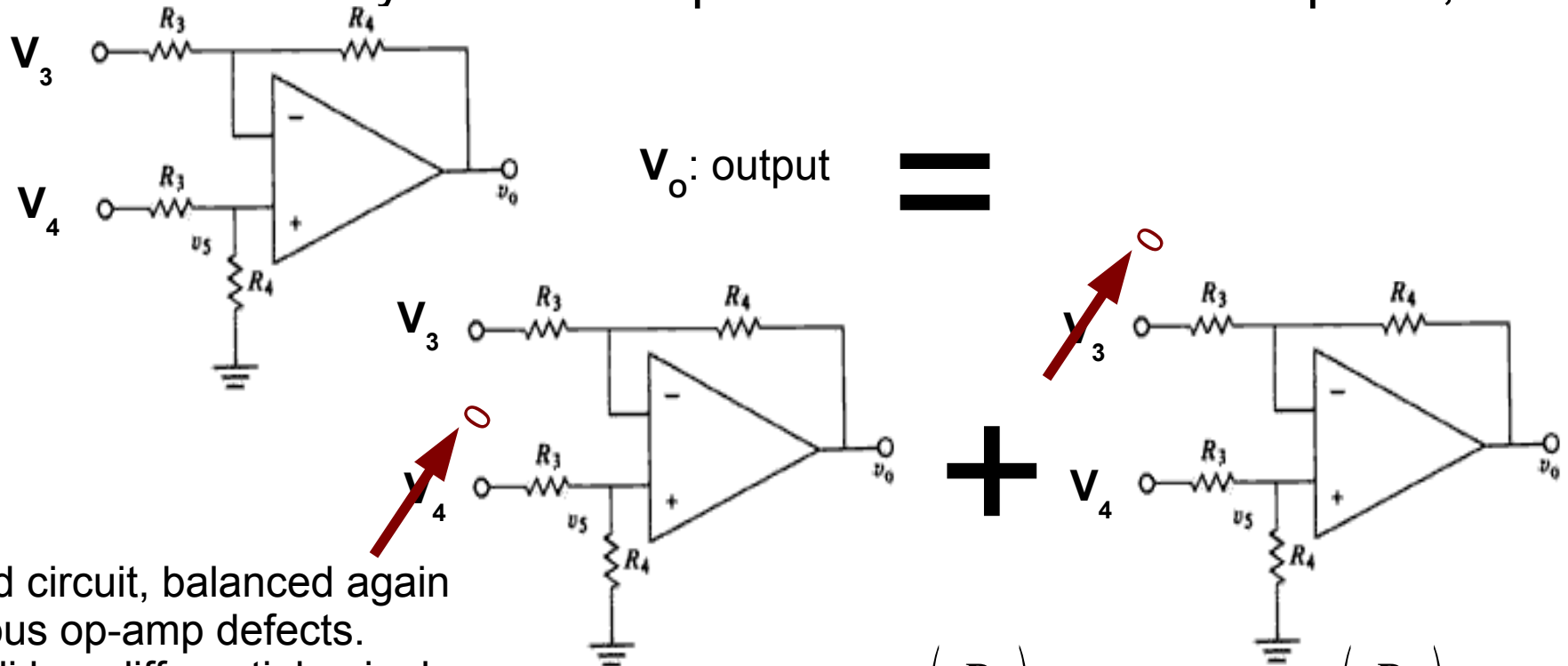Based on our analysis of each part of the difference amplifier,



Good circuit, balanced again
various op-amp defects.
Ampli has differential gain, but no
common mode gain.

Disadvantages:

- need good matching R_3, R_4
- input impedance is low ($=R_3$)



$$V_o = -\left(\frac{R_4}{R_3}\right) V_3 + \left(\frac{R_4}{R_3}\right) V_4$$

$$V_o = \left(\frac{R_4}{R_3}\right) (V_4 - V_3)$$

Amplifiers

Slide 03B.11

The instrumentation amplifier

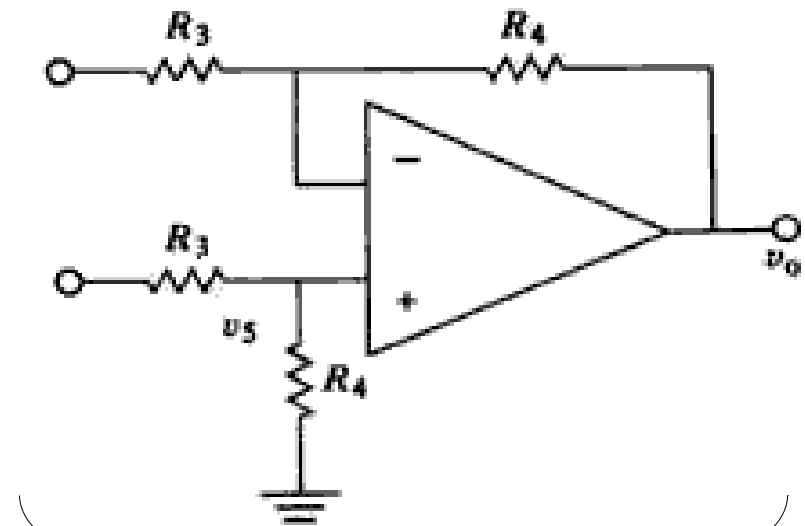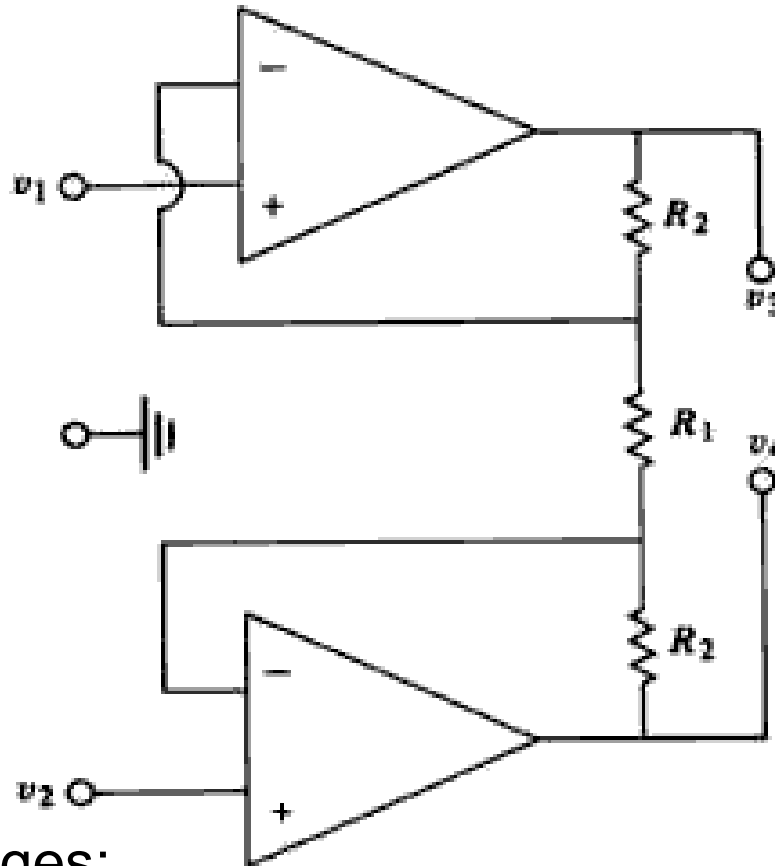

Difference Amplifier

Advantages:

- High input impedance
- Matched components (available in chip form). Stable time/temp/freq
- Gain controlled by selection of R_1

Amplifiers

Slide 03B.12

The instrumentation amplifier

In both input op-amps, $V_- = V_+$, since we have negative feedback.

Thus, we can analyse current i

$$i = \frac{V_+ - V_-}{R_G}$$

$$V_3 - V_4 = (R_G + 2R_2)i$$


$$V_3 - V_4 = \frac{R_G + 2R_2}{R_G} (V_+ - V_-)$$

$$V_3 - V_4 = \left(1 + 2\frac{R_2}{R_G}\right) (V_+ - V_-)$$

Using the equation for the difference amplifier, we have

$$V_o = \frac{R_4}{R_3} (V_3 - V_4)$$
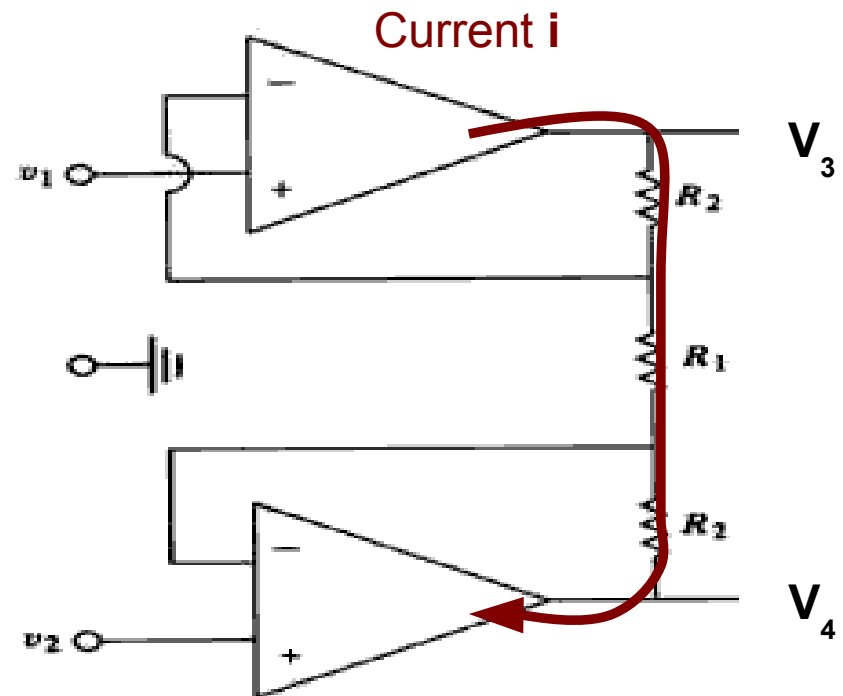
$$V_o = \left(1 + 2\frac{R_2}{R_G}\right) \left(\frac{R_4}{R_3}\right) (V_+ - V_-)$$



Amplifiers

Slide 03B.13

Instrumentation Amplifiers



Low Cost, Low Power Instrumentation Amplifier

AD620

FEATURES

EASY TO USE

Gain Set with One External Resistor
(Gain Range 1 to 1000)

Wide Power Supply Range (± 2.3 V to ± 18 V)

Higher Performance than Three Op Amp IA Designs

Available in 8-Lead DIP and SOIC Packaging

Low Power, 1.3 mA max Supply Current

EXCELLENT DC PERFORMANCE ("B GRADE")

50 μ V max, Input Offset Voltage

0.6 μ V/ $^{\circ}$ C max, Input Offset Drift

1.0 nA max, Input Bias Current

100 dB min Common-Mode Rejection Ratio (G = 10)

LOW NOISE

9 nV/ $\sqrt{\text{Hz}}$, @ 1 kHz, Input Voltage Noise

0.28 μ V p-p Noise (0.1 Hz to 10 Hz)


EXCELLENT AC SPECIFICATIONS

120 kHz Bandwidth (G = 100)

15 μ s Settling Time to 0.01%

CONNECTION DIAGRAM

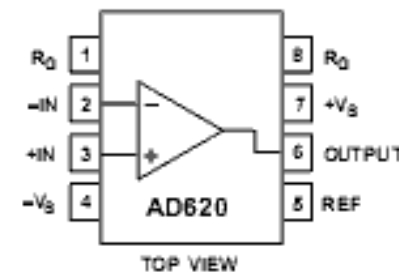8-Lead Plastic Mini-DIP (N), Cerdip (Q)
and SOIC (R) Packages



Spec sheet from: analog devices

Amplifiers

Slide 03B.14

Questions

What are some requirements for medical amplifiers?

What is the CM signal? Why is it a problem?

Why are single chip instrumentation amplifiers better than 3 op-amp ones?

From the spec sheet: The internal gain resistors, R1 and R2, are trimmed to 24.7 k Ω , allowing the gain to be programmed with a single external resistor: $G = 1 + 49.4\text{k}\Omega/R_G$. What is R3, R4?

Exam 07f (1c) Because the scalp is an insulator, the EEG signal levels are small, and high amplification is required. Consider an EEG signal which causes a difference of 15 μV between two electrodes. The neon interrogation lights cause a common mode signal of 1.8V on the scalp. Given an instrumentation amplifier with gain 10 and CMRR=80 dB, what level of common mode and difference signal will be measured?

Will twisting the EEG lead wires together help to reduce the interference from the lights?