

Biopotential Amplifiers: Circuits

- Circuit examples from Spec Sheet
Analog Devices AD620 Instrumentation Amplifier
www.datasheetcatalog.org/datasheet/analogdevices/105505445AD620_e.pdf

Single supply pressure transducer

Driven Right leg circuit

Amplifier Circuits

Grounding: Analog vs. Digital

Single supply operation

Driven Ground

Wheatstone bridge

Issues in biomedical Amplifiers


Filtering for powerline noise

Bioimpedance Measurement

Amplifier Circuits

Slide 03D.2

Pressure Sensor circuit

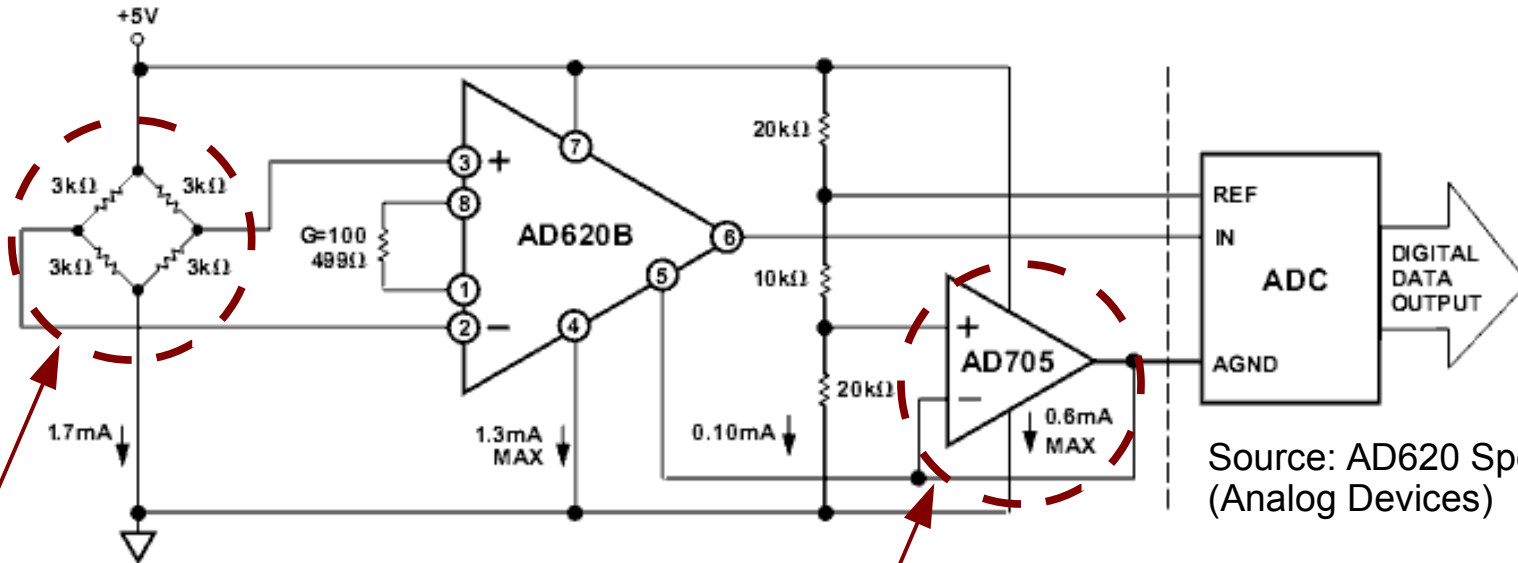

Source: AD620 Spec sheet
(Analog Devices)


Figure 35. A Pressure Monitor Circuit which Operates on a +5 V Single Supply

Wheatstone
Bridge Circuit

Single Supply
configuration

Analog Ground

Wheatstone bridge

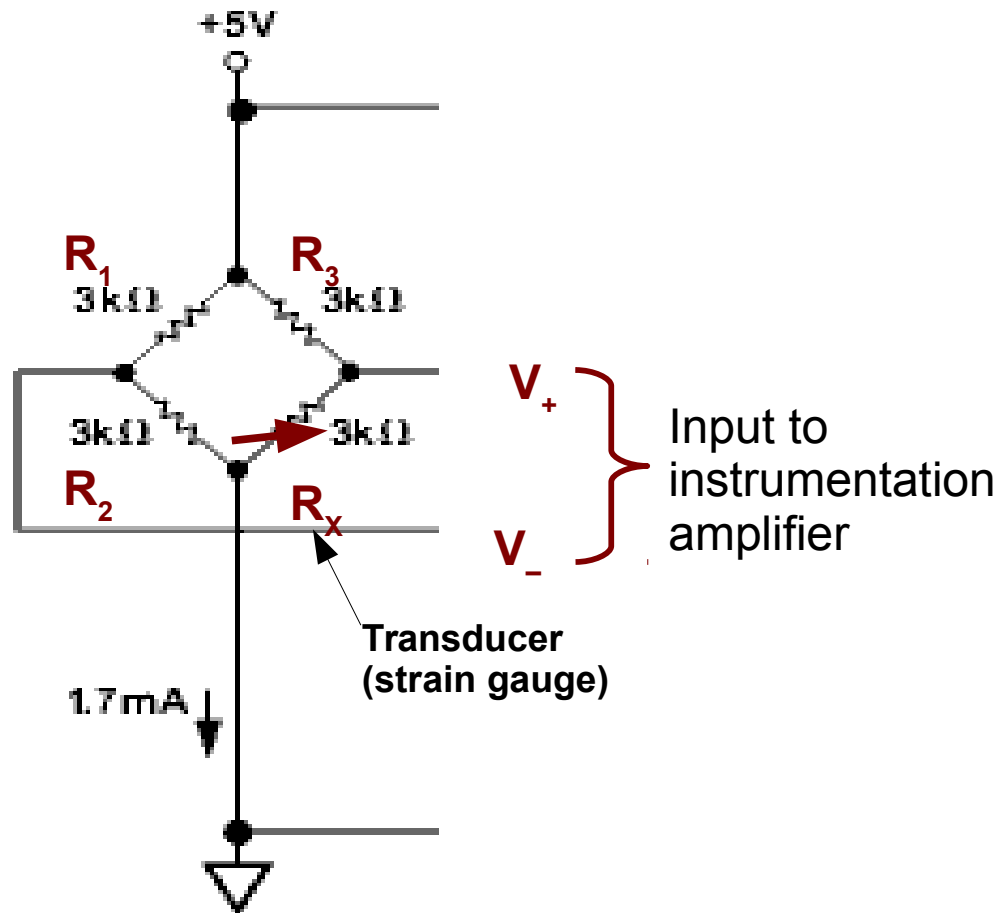

The Wheatstone bridge is a popular measurement instrument.

$$V_+ = \frac{R_2}{R_1 + R_2}$$

$$V_- = \frac{R_x}{R_3 + R_x}$$

$$V_+ - V_- = \frac{R_x}{R_3 + R_x} - \frac{R_2}{R_1 + R_2}$$


Choose: $R_1 = R_3$ $R_x = R_2 + \Delta$

$$V_+ - V_- = \frac{R_2 + \Delta}{R_1 + R_2 + \Delta} - \frac{R_2}{R_1 + R_2}$$

$$V_+ - V_- \approx \frac{\Delta}{R_1 + R_2}$$

The advantage is that it autocalibrates for time/temperature variations

Wheatstone bridge: Question

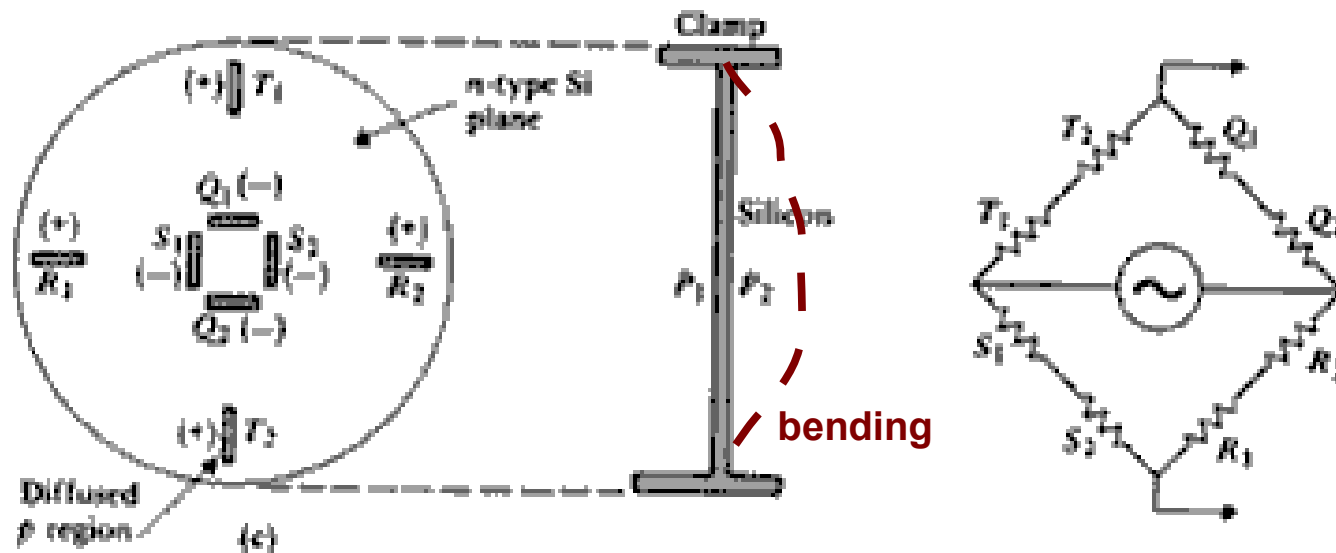

Consider a strain gauge instrumented pressure transducer

- Before bending $T_1 = T_2 = R_1 = R_2 = Q_1 = Q_2 = S_1 = S_2 = 1\text{k}\Omega$. What is output voltage?
- Hot fluid increases all resistances by 10%. What is output voltage?
- During bending $T_1 = T_2 = R_1 = R_2$ increase by 1% and $Q_1 = Q_2 = S_1 = S_2$ by 0.1%. What is output voltage?
- Hot fluid now increases resistances by 10%. What is output voltage?

Amplifier Circuits

Slide 03D.5


Analog Grounds

Adequate grounding is extremely important for good amplifier performance.

Any noise on the ground will become part of the output signals.

A short list of things to be careful of:

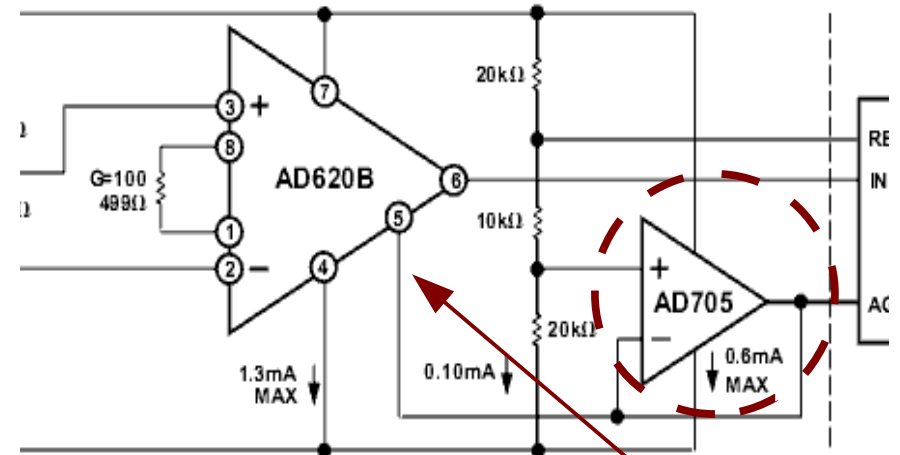- Keep analog and digital grounds separate. Digital grounds have large switching transients which put noise onto supply and ground.
- Join analog and digital grounds at only one point. This avoids “ground loops” which can be magnetic pick-ups for line noise.
- Use lots of bypass capacitors on chip power supplies. Use both ceramic (nF range) and electrolytic (μF range).



Analog Ground.

$$V+ = 5V \frac{20k}{(20k+10k+20k)} = 2V$$


The circuit is a unity gain follower. The value of the follower: the output impedance is much lower, so it can source current without a drop in voltage.

I would put capacitors (a few 100nF of ceramics) on the input and output.

Amplifier Circuits

Slide 03D.6

Single Supply Design

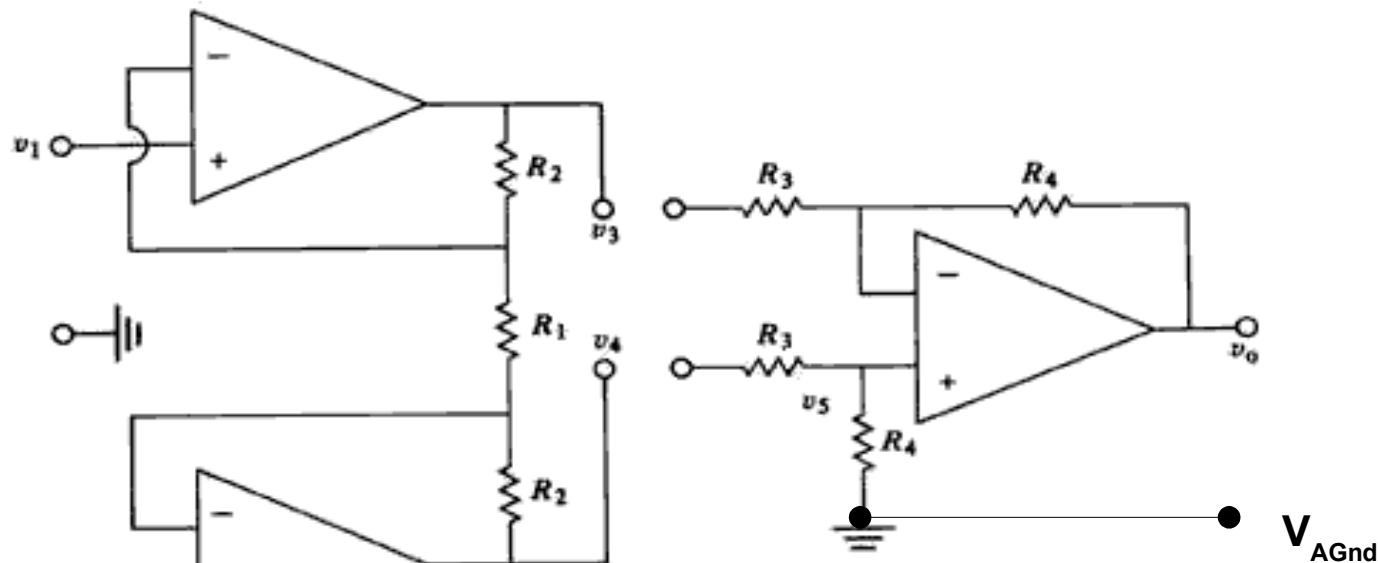

Instead of ground, we connect
to the Analog Gnd level (=Signal Ground)

Due to linearity, we can shift the voltage level

$$V_O = A(V_4 - V_3), \text{ where } A = R_4/R_3$$

Replace $V = V' - V_{AGnd}$ (since reference level is arbitrary)

$$V_O' - V_{AGnd} = A((V_4' - V_{AGnd}) - (V_3' - V_{AGnd}))$$

$$V_O' = A(V_4' - V_3') + V_{AGnd}$$

Amplifier Circuits


Slide 03D.7

Single Supply Design

Single supply design allows circuits to run off a single voltage supply, typically 0 and 5V. Signal levels need to be kept in the centre of the supply range (at around 2 – 2.5V) and away from amplifier limits.

SS design is common in hand held devices. It uses a single battery

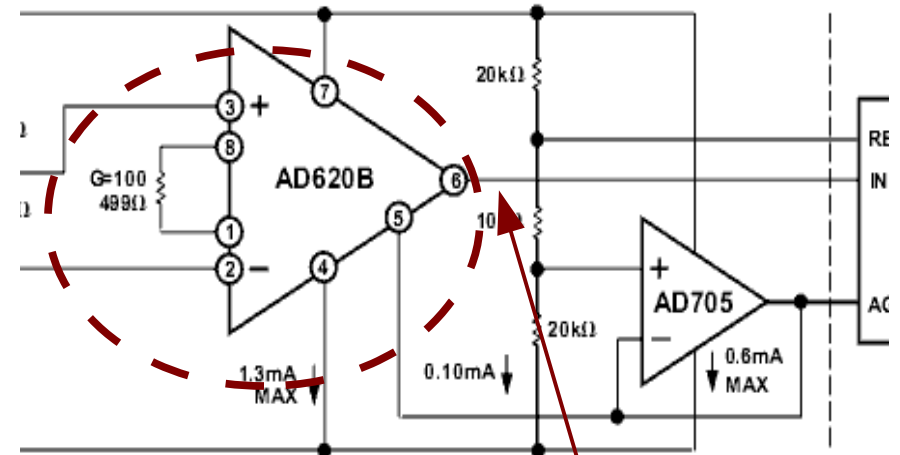- Cheaper to manufacture and use
- Lower power consumption.



Gain calculation

$$A = 49.4k/R_G + 1$$
$$= 49.4k/0.499 + 1 = 100$$


So

$$V_o = 100(V_+ - V_-) + 2V$$

Amplifier Circuits

Slide 03D.8

ECG Monitoring circuit

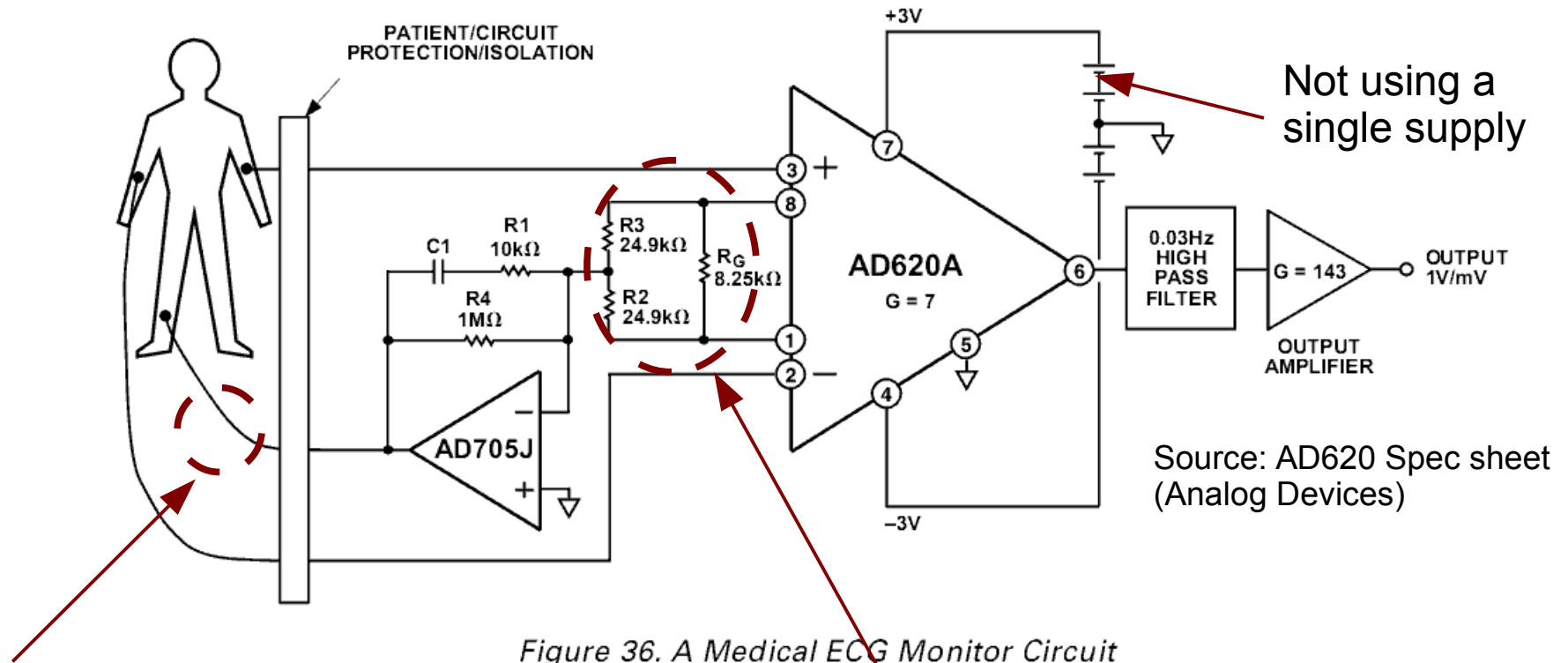


I would put a resistor in this Line, for patient protection (may be in protection/isolation circuit)

Driven Ground Circuit

Gain is
 $R_G = (24.9k + 24.9k) || 8.25k$
 $R_G = 7.08k$

$$A = 49.4k / 7.08k + 1 = 8$$

Driven Right Leg circuit

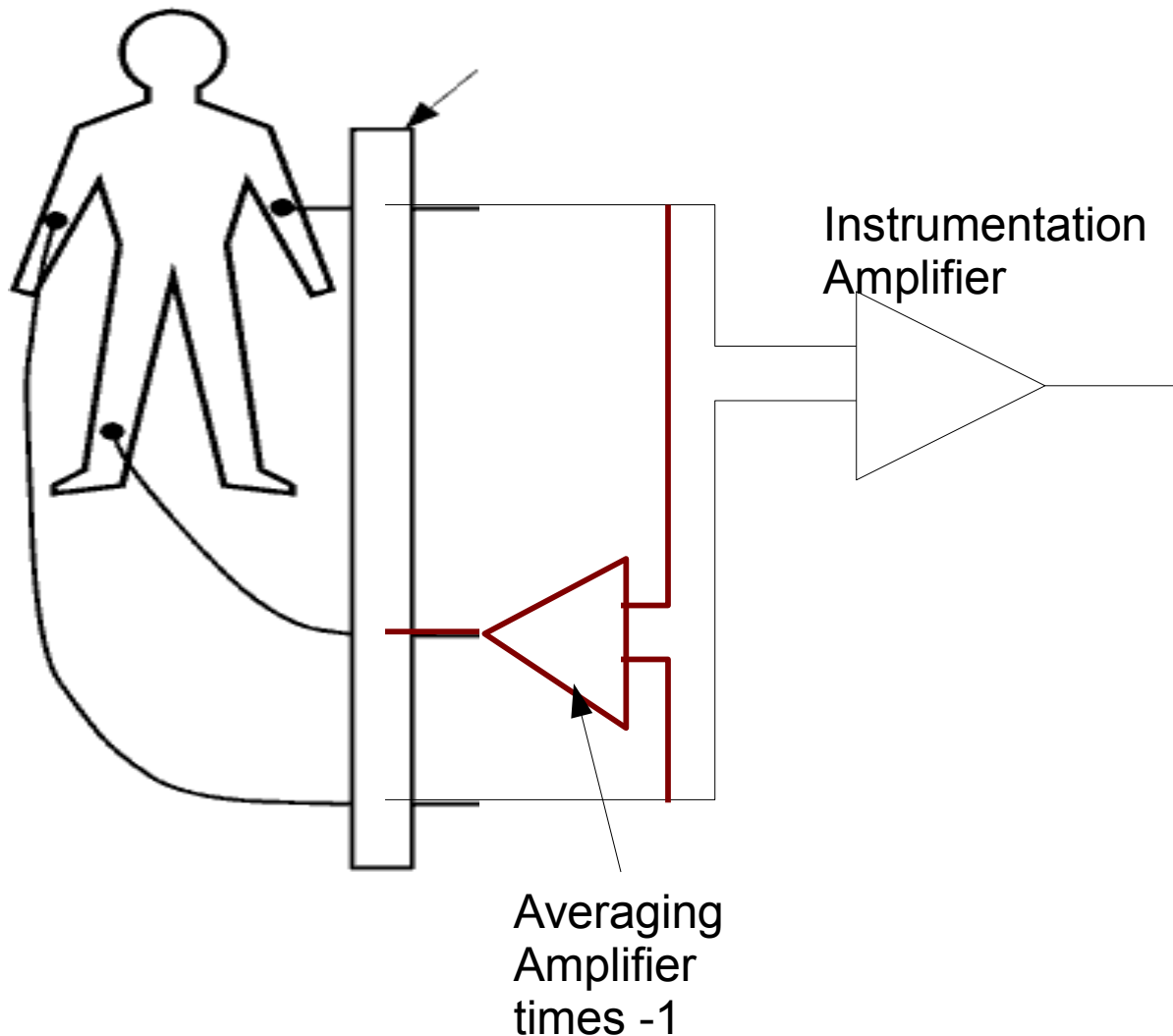

Idea: if CMRR is such a problem, why don't we just force it to ground.

So we measure the V_{cm} , by averaging V_+ and V_- .

Next we build a negative feedback loop to drive V_{cm} to zero.

The driven right leg circuit also provides some safety (driving high voltages to zero ... but limited by transistor breakdown)


Driven Right Leg circuit

Why right leg?

Looking at the heart, the dominant electrical fields are generated away from the right leg.

Also, for Einthoven's leads

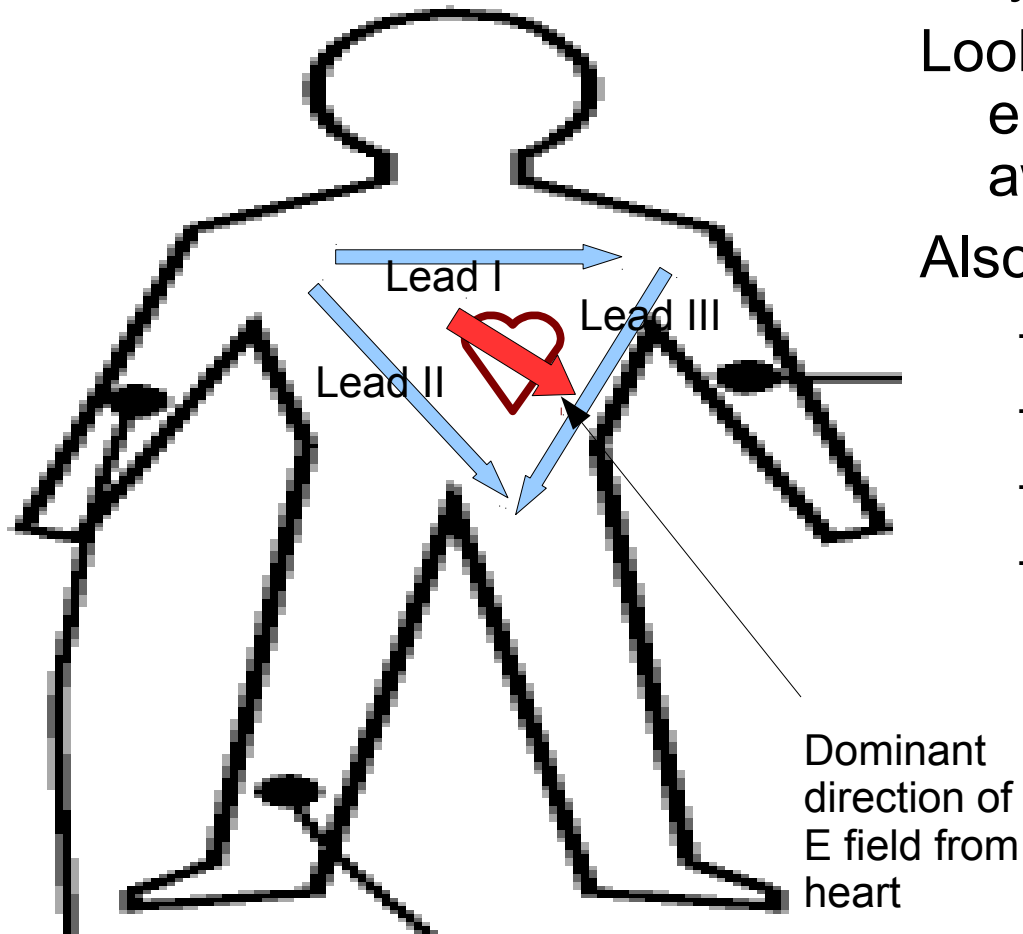
- Lead I: RA \rightarrow LA
- Lead II: RA \rightarrow LL
- Lead III: LA \rightarrow LL
- Thus, only the RL is left unused for the diagnostic information



Amplifier Circuits

Slide 03D.11

Analysis of Driven Leg gain

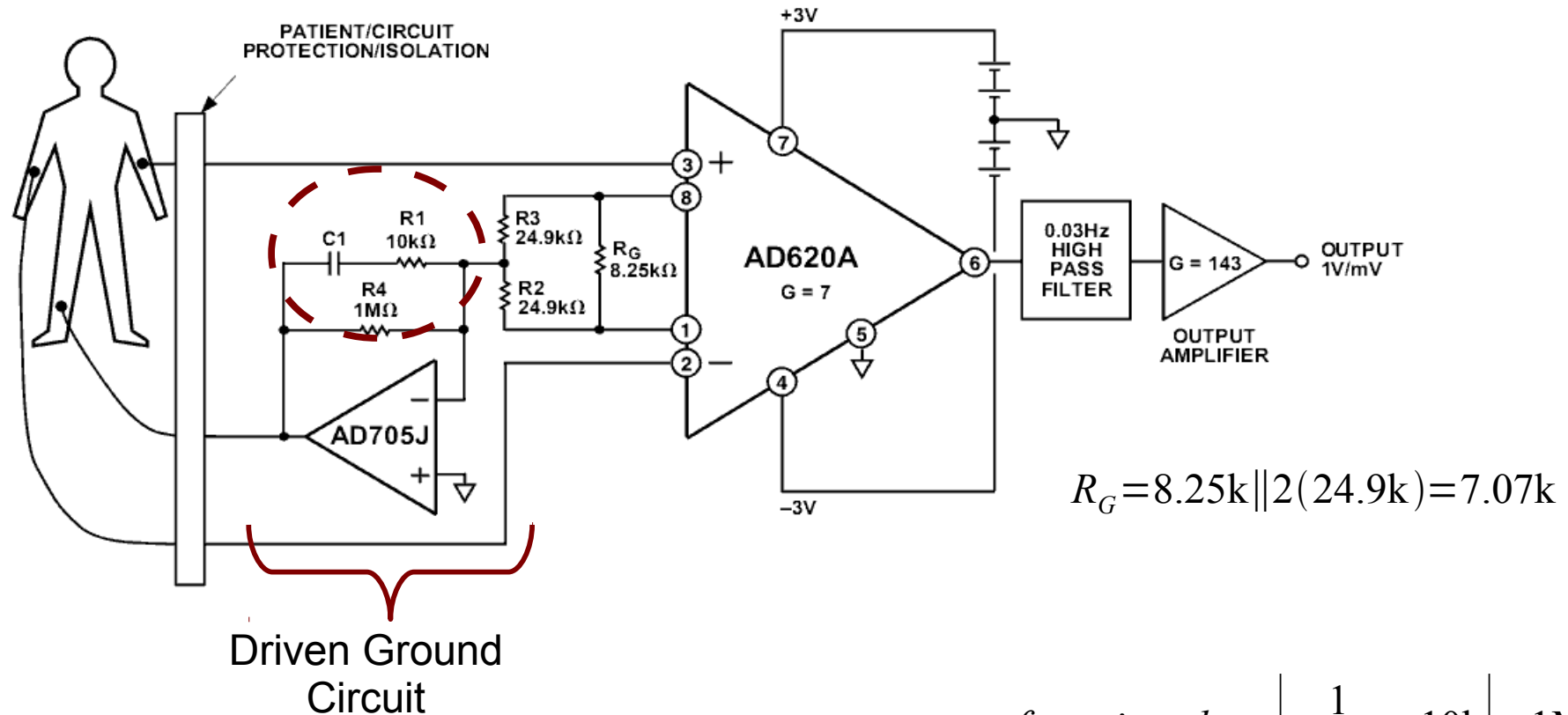

$$DC \text{ Gain} = \frac{-R_4}{R_3} = -\left(\frac{1M}{24.9k \parallel 24.9k}\right) = -80$$

$$AC \text{ Gain} = \frac{-R_4}{R_3} = -\left(\frac{1M \parallel 10k}{24.9k \parallel 24.9k}\right) = -0.8$$

AC |gain| < 1
to prevent
oscillations

f_b point when: $\left| \frac{1}{j\omega C} + 10k \right| = 1M$

$$\sqrt{\frac{1}{(\omega C)^2} + 10k^2} = 1M$$

$$\omega = (C \sqrt{1M^2 - 10k^2})^{-1} = (C \times 995k)^{-1}$$

Components of a medical ECG amplifier

Functional Blocks

- Protection Circuits
- Isolation Circuits
- Lead selector
- Calibration signal
- Preamplifier (with high CMRR)
- Main amplifier (with settable gain)
- Driven RL circuit
- Analog to Digital Converter
- Memory
- Local display
- Upload / link to hospital IT system

And if the unit is wireless, then there are still more components required:

- Battery, wireless LAN connection, security, local storage & upload for when LAN not available ...

Issues in medical amplifiers

Saturation (clipping) of signal

- gain larger than ADC limits

Ground loops

Open lead wires



Large signal transients

- Transient protection required on all inputs, usually using zener diodes (or for smaller signals, back to back Si diodes)

Power line interference

- Can remove with analog filters (60Hz notch filter) in the device, or in post processing
- Post-processing: use a strategy of modelling and subtraction

Interference from other devices

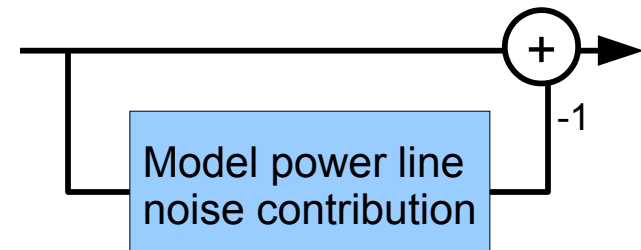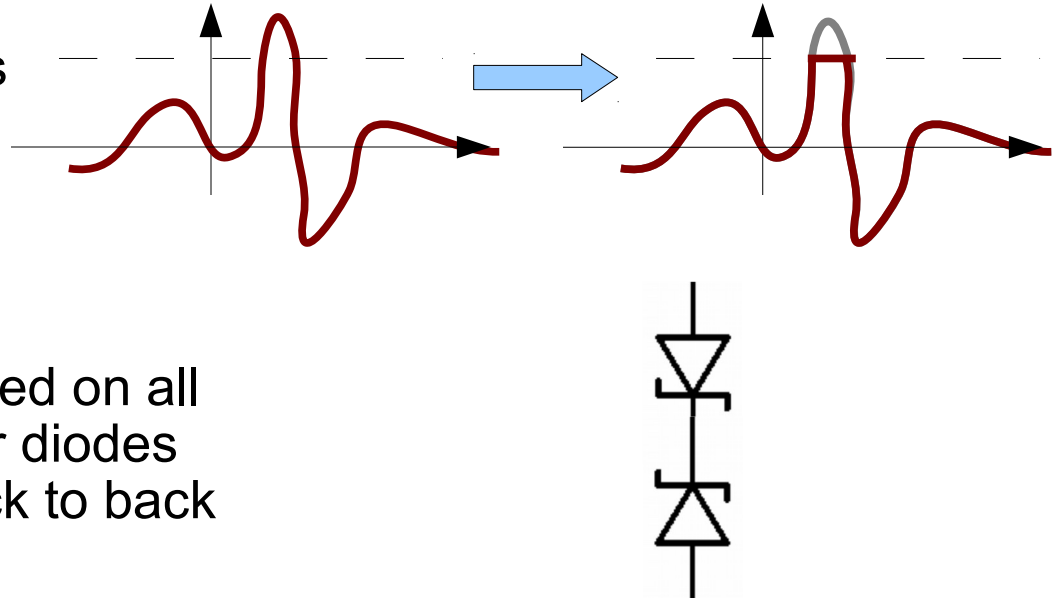

Questions

- Draw a Wheatstone bridge circuit. What types of circuit changes does it provide resistance against?
- In what situations is single supply design a good idea? Sketch a block diagram of a single supply amplifier.
- What is CMRR? Why is it a problem in medical instrumentation? What kinds of interference causes a large CM signal?
- Sketch a block diagram of a driver right leg circuit?
- How does a driver right leg circuit help improve CM response?
- What causes signal saturation (clipping)? How can you detect it?
- Describe how an infusion pump near a biomedical amplifier can cause power line interference. Describe some strategies to remove power line interference.
- What is a problem with open lead lines into an amplifier?