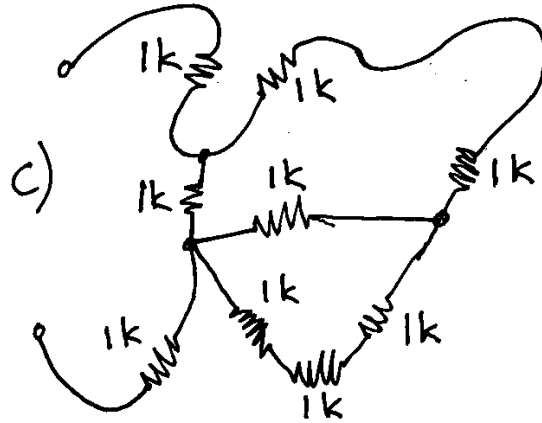
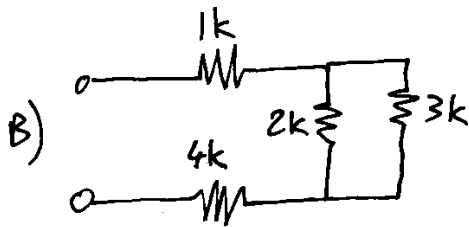
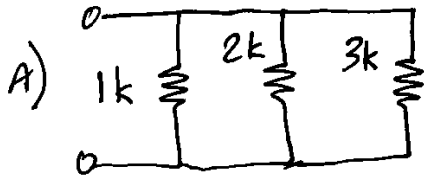
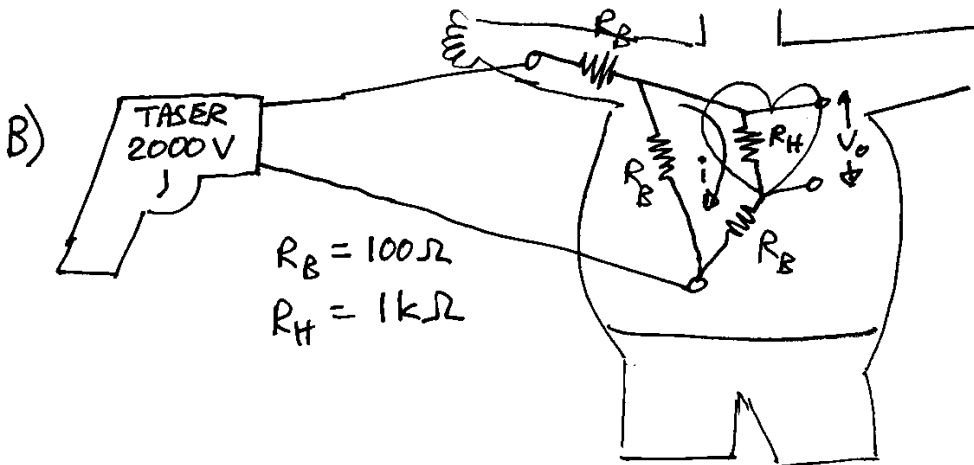
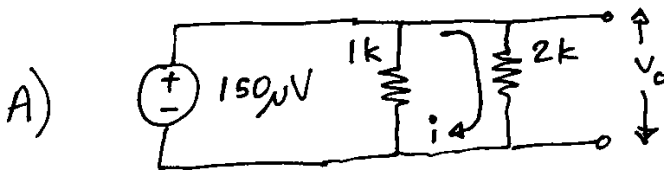





Tutorial #1: Page #1

① Find Equivalent Resistor

② Find V_o and i using Equivalent Resistances

Tutorial #1: Page #2

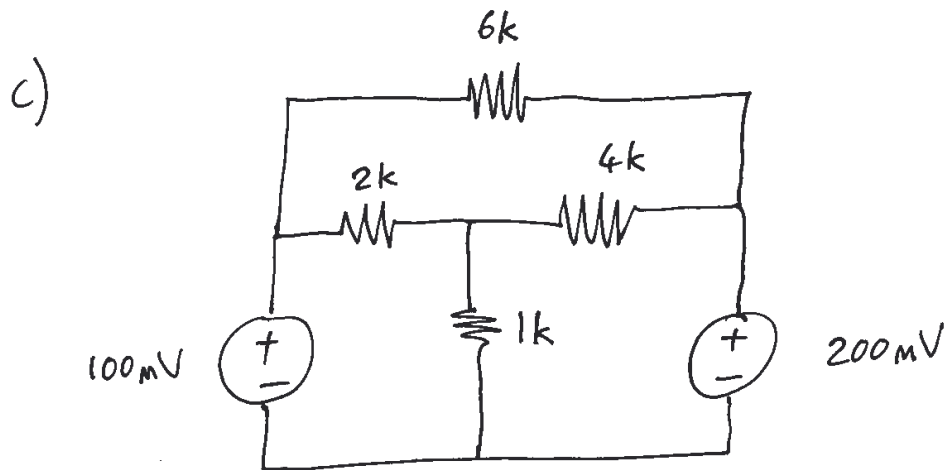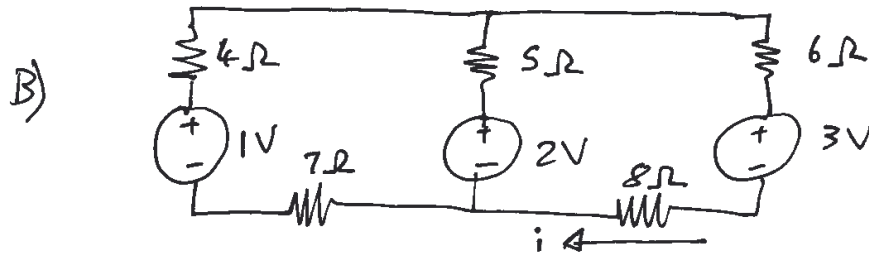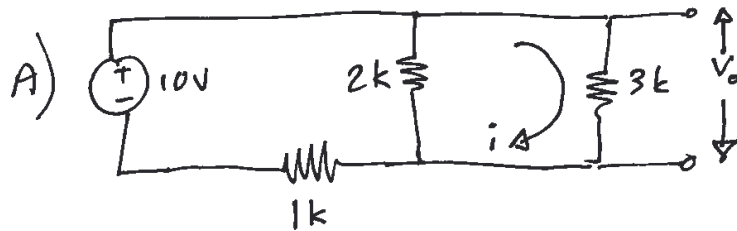③ Solve for i and V_o using KVL and KCL
write loops and equations



1A $R = 1k \parallel 2k \parallel 3k$

1B $R = 1k + (2k \parallel 3k) + 4k$

1C $R = 1k + (1k \parallel (1k + 1k + (1k \parallel (1k + 1k + 1K)))) + 1k$


2A $V_o = 150\mu V$
 $i = \frac{150\mu V}{2k\Omega}$

2B Define point x with V_x at armpit
 Equivalent Resistance, R_{eq} , from V_x to bottom
 $R_{eq} = R_B \parallel (R_H + R_B)$
 Voltage divider: $V_x = \frac{R_{eq}}{R_{eq} + R_B}$
 $i = \frac{V_x}{R_B + R_H}$
 $V_o = iR_H$


3A Define loop current in left (i_l) and right ($i_r = i$) loop
 KVL for i_l : $+10V - 2k(i_l - i_r) - 1k(i_l) = 0$
 KVL for i_r : $-2k(i_r - i_l) - 3k(i_r) = 0$
 $2k(i_r - i_l) + 3k(i_r) = 0$
 $2k(i_r) + 3k(i_r) = 2k(i_l)$
 $5k(i_r) = 2k(i_l)$
 $i_l = 2.5i_r$
 KVL #1: $10V = 2k(i_l - i_r) + 1k(i_l)$
 $10V = 2k(2.5i_r - i_r) + 1k(2.5i_r)$
 $10V = 5.5ki_r$

Tutorial #2Find V_o and i


A)

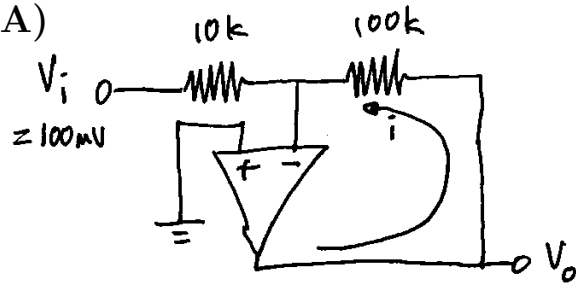


B)

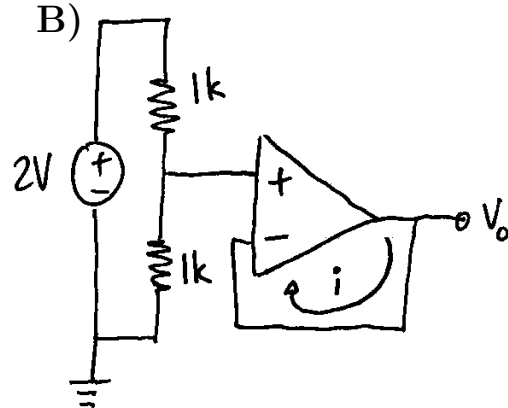


C)

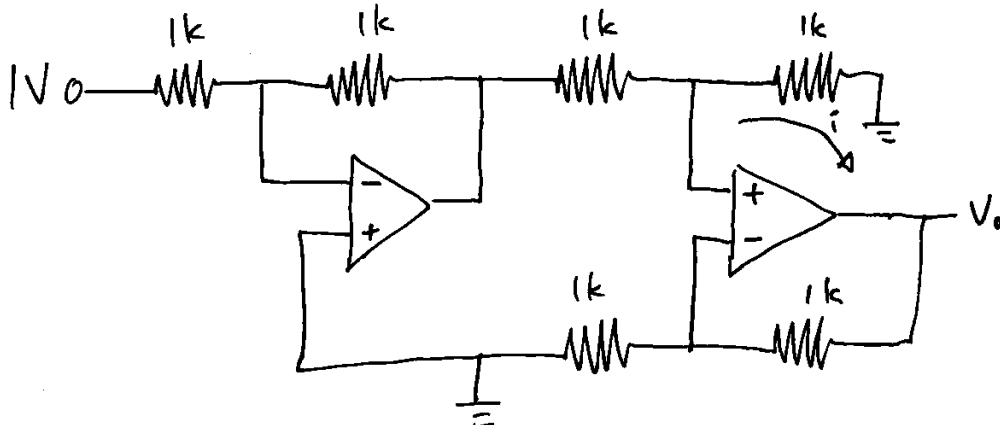

D)

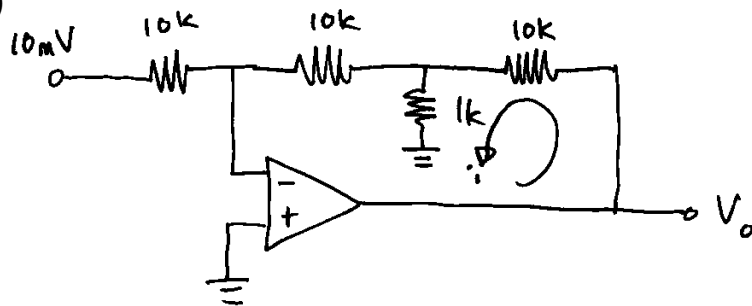

E)

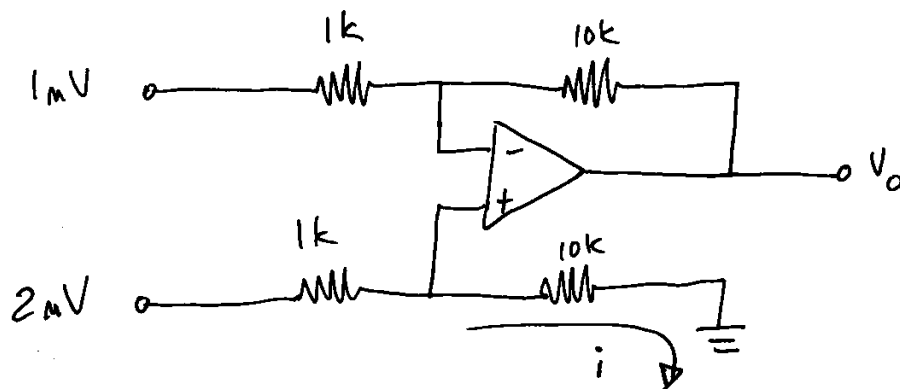

A $V_o = -\frac{100k}{10k} 100\mu V$
 $i = \frac{V_o}{100k}$

B Voltage divider, then buffer
 $V_o = \frac{1k}{1k+1k} 2V$

C Output of first op-amp: V_x
 $V_x = -\frac{1k}{1k} 1V = -1V$
2nd op-amp, $V_+ = \frac{1k}{1k+1k} V_x = -0.5V$
 $i = \frac{V_x}{1k+1k} = -0.5mA$
 $V_o = (1 + \frac{1k}{1k}) V_+ = 2(-0.5V) = -1V$

Tutorial #3

