

**Question 1: Voltage dividers**

With Reference to Figure 1, write down the expressions for the voltages across R1 and R2.

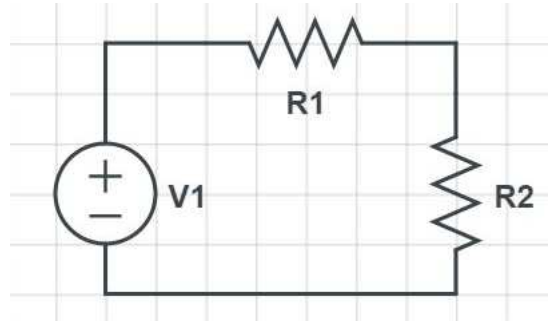


Figure 1

If  $V1 = 11V$ ,  $R1 = 220\Omega$  and  $R2 = 330\Omega$

- a) Calculate the voltage across R1

$$V1 \frac{R1}{R1 + R2} = 11V \frac{220}{550} = 4.4V$$

- b) Calculate the current supplied by the source

$$I = \frac{V1}{R1 + R2} = \frac{11V}{550\Omega} = 20 \text{ mA}$$

- c) If we wish to replace R1 and R2 with a single resistor, what should its value be?

$$R = R1 + R2 = 550\Omega$$

**Question 2: Kirchhoff's current laws and Resistors in parallel**

Referring to Figure 2 and using  $V_1 = 11\text{V}$ ,  $R_1 = 220\Omega$  and  $R_2 = 330\Omega$

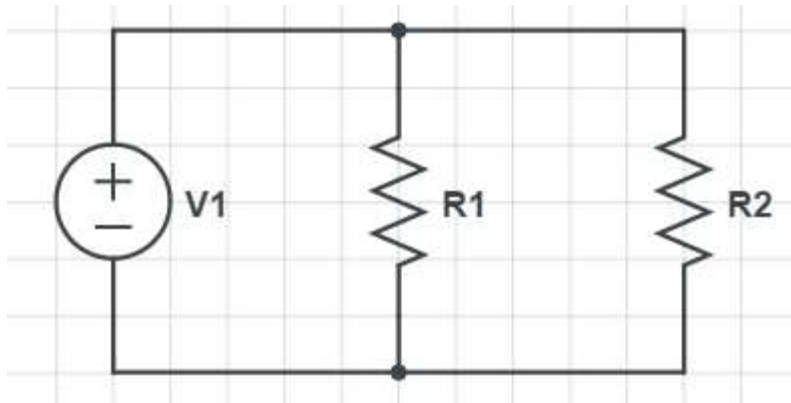


Figure 2

- a) What is the total current supplied by the source?

$$I = I_1 + I_2 = \frac{V_1}{R_1} + \frac{V_1}{R_2} = \frac{11\text{V}}{220\Omega} + \frac{11\text{V}}{330\Omega} = 83.3 \text{ mA}$$

- b) What is the voltage across R2?

$$V_1 = 11\text{V}$$

- c) If we wish to replace R1 and R2 with a single resistor, what should its value be?

$$\frac{1}{R} = \frac{1}{220\Omega} + \frac{1}{330\Omega} \Rightarrow R = 132 \Omega$$

**Question 3: Series-parallel circuit**

In Figure 3 below find  $I_o$  in the circuit below using basic circuit theory.

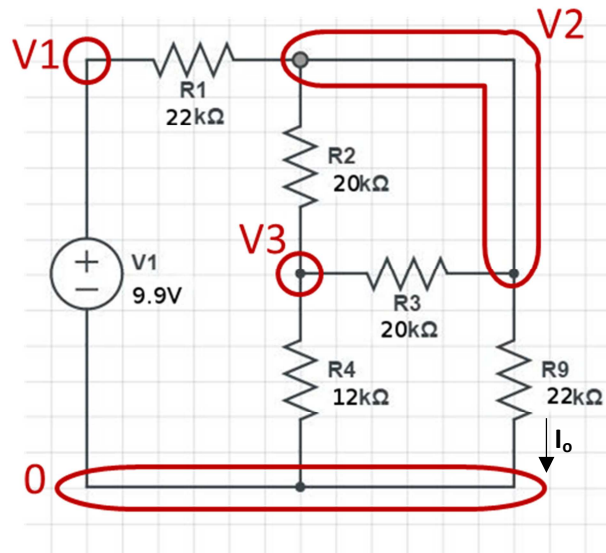


Figure 3

Using formal nodal analysis:

$$\text{Node 2: } \frac{V_1 - V_2}{R_1} - \frac{V_2 - V_3}{R_2} - \frac{V_2 - V_3}{R_3} - \frac{V_2 - 0}{R_9} = 0$$

$$\text{Node 3: } \frac{V_2 - V_3}{R_2} - \frac{V_3 - V_2}{R_3} - \frac{V_3 - 0}{R_4} = 0$$

Collecting terms:

$$\frac{V_1}{R_1} - V_2 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_9} \right) + V_3 \left( \frac{1}{R_2} + \frac{1}{R_3} \right) = 0$$

$$V_2 \left( \frac{1}{R_2} + \frac{1}{R_3} \right) - V_3 \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) = 0$$

Eliminating  $V_3$ :

$$V_2 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_9} \right) - V_2 \frac{\left( \frac{1}{R_2} + \frac{1}{R_3} \right)^2}{\left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)} = \frac{V_1}{R_1}$$

$$I_o = \frac{V_2}{R_9} = \frac{V_1}{R_1 R_9} \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_9} - \frac{\left( \frac{1}{R_2} + \frac{1}{R_3} \right)^2}{\left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)} \right]^{-1}$$

$$= \frac{V_1}{R_1 R_9} \left[ \frac{1}{R_1} + \frac{1}{R_9} + \left( \frac{1}{R_2} + \frac{1}{R_3} \right) \left[ 1 - \frac{1}{1 + \frac{1/R_4}{1/R_2 + 1/R_3}} \right] \right]^{-1}$$

$$= \frac{9.9V}{22k \cdot 22k} \left[ \frac{1}{22k} + \frac{1}{22k} + \left( \frac{1}{20k} + \frac{1}{20k} \right) \left[ 1 - \frac{1}{1 + \frac{1/12}{1/20 + 1/20}} \right] \right]^{-1}$$

$$= \frac{9.9V}{22k \cdot 22k} \left[ \frac{1}{22k} + \frac{1}{22k} + \frac{1}{10k} \left[ 1 - \frac{1}{1 + \frac{10}{12}} \right] \right]^{-1} = \frac{9.9V}{22k \cdot 22k} \left[ \frac{3}{22k} \right]^{-1}$$

finally giving

$$I_o = \frac{9.9V}{22k \cdot 22k} \frac{22k}{3} = 0.15 \text{ mA}$$

(ugh!).

By inspection:

The RHS of the circuit simplifies to

$$(R_2 \parallel R_3 + R_4) \parallel R_9 = (20k \parallel 20k + 12k) \parallel 22k = 22k \parallel 22k = 11k$$

Hence the total current from the source is

$$\frac{V_1}{R_1 + (R_2 \parallel R_3 + R_4) \parallel R_9} = \frac{9.9V}{22k + 11k} = 0.3 \text{ mA}$$

of which exactly half flows through  $R_9$ .

Hence  $I_o = 0.15 \text{ mA}$  as before (much easier!)

**Question 4: Capacitors**

In Figure 4, a capacitor of value  $C_1 = 33\text{nF}$  and  $C_2 = 220\text{nF}$  are charged to voltage  $V_1 = 4\text{V}$

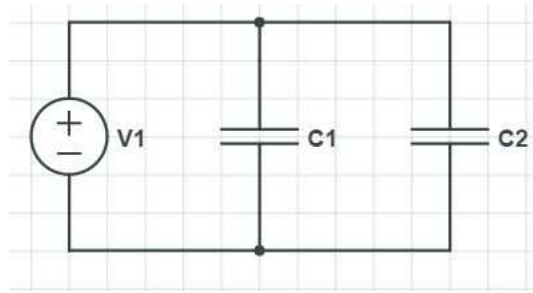


Figure 4

- a) What is the charge on each capacitor?

$$Q_1 = C_1 V_1 = (33\text{nF})(4\text{V}) = 1.32 \times 10^{-7} \text{ coulomb}$$

$$Q_2 = C_2 V_1 = (220\text{nF})(4\text{V}) = 8.8 \times 10^{-7} \text{ coulomb}$$

- b) Write down an expression's for the net capacitance of a number of capacitors in series and a number of capacitors in parallel.

$$\text{Series: } \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

$$\text{Parallel: } C = C_1 + C_2 + \dots + C_n$$

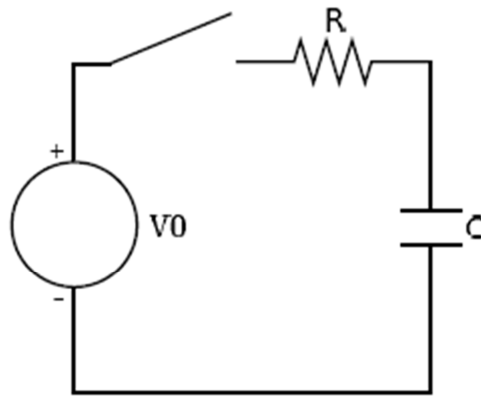
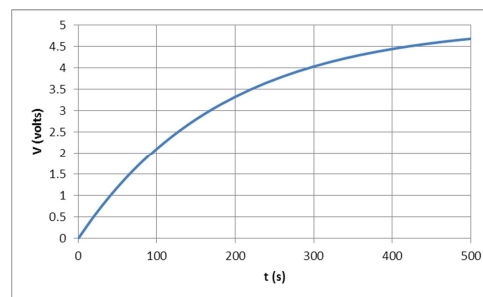
**Question 5: Charging Capacitor**

Figure 5

- a) At time  $t = 0$  a switch is closed, connecting a voltage source  $V_0 = 5V$  through resistor  $R = 47k$  to a capacitor  $C = 3900\mu F$ . Sketch the voltage across the capacitor as a function of time. Show approximate times on the horizontal axis.



- b) What will the voltage across the Resistor be after 100 milliseconds?

Since  $100 \text{ ms} \ll \tau$ , the capacitor will be essentially uncharged at this time i.e. to a very good approximation,  $V_C = 0V$  and  $V_R = 5V$ . We could calculate it exactly using

$$V_R = 5 - V_C = 5e^{-t/RC}$$

with  $RC = (47k)(3900\mu F) = 183.3 \text{ s}$ ,  $V_R = 5e^{-(0.1/183.3)} = 4.997V$

- c) Calculate the 10%-90% rise time.

$$0.1V_0 = V_0 \left(1 - e^{-t_1/RC}\right)$$

$$0.9V_0 = V_0 \left(1 - e^{-t_2/RC}\right)$$

Dividing by  $V_0$  and rearranging,

$$0.9 = e^{-t_1/RC}$$

$$0.1 = e^{-t_2/RC}$$

or (dividing top by bottom)

$$t_2 - t_1 = RC \ln 9$$

With  $RC = 183.3 \text{ s}$ ,  $t_2 - t_1 = 402.75 \text{ s}$