


(1/5) Name \_\_\_\_\_ Student Number \_\_\_\_\_

(4/5) Please answer the following question in the space below:

For the electronic diagram shown,  $V_{CC} = 6\text{ V}$ ,

- $R_1 = R_2 = 10\text{ k}\Omega$ , and  $C_1 = 10\text{ nF}$ .  
Sketch the waveforms at R, S, Q,  $\bar{Q}$ , and pin #2.

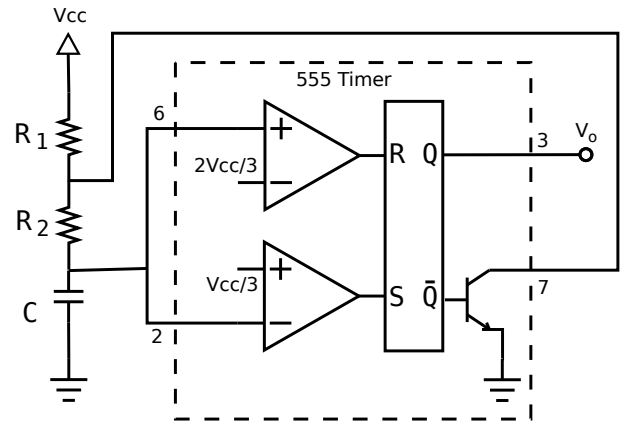Label voltages and transition times. Show the first two periods of the oscillation. At  $t = 0$ , the capacitor has zero charge.




(1/5) Name \_\_\_\_\_ Student Number \_\_\_\_\_

(4/5) Please answer the following question in the space below:

For the electronic diagram shown, the op amp is ideal, with  $V_{CC} = 5\text{ V}$ . It is desired to have an oscillation frequency of  $10\text{ kHz}$ .

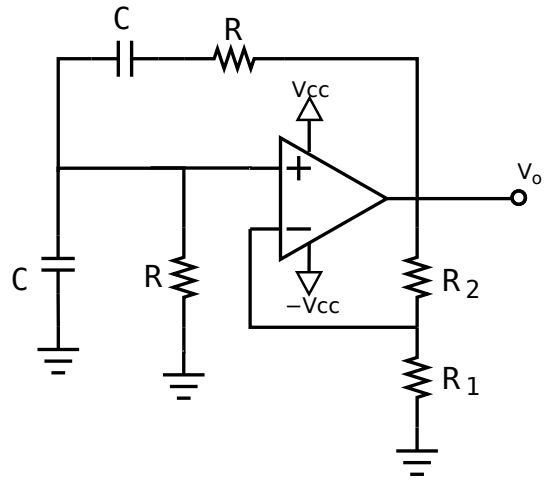- If  $C_1 = 10\text{ nF}$ , what value of  $R$  is required?
- If  $R_1 = 10\text{ k}\Omega$ , what value of  $R_2$  is required?




(1/5) Name \_\_\_\_\_ Student Number \_\_\_\_\_

(4/5) Please answer the following question in the space below:

For the electronic diagram shown, the op amp is ideal, with  $V_{CC} = 5\text{ V}$ .  $C_1 = 10\text{ nF}$ ,  $R = 10\text{ k}\Omega$ ,  $R_1 = 1\text{ k}\Omega$ , and  $R_2 = 10\text{ k}\Omega$ , and

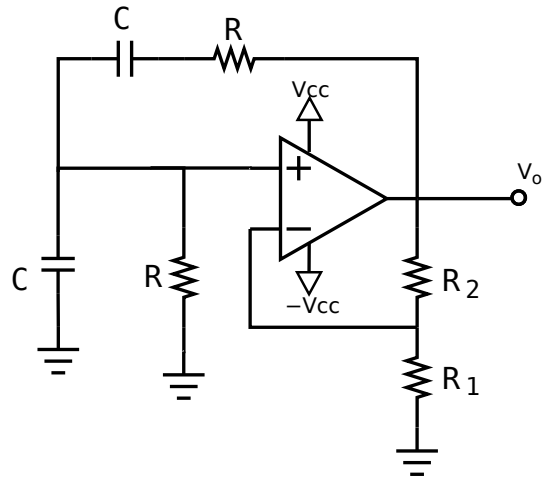- What is the frequency of the waveform at  $V_o$ ?
- Sketch the shape of  $V_o$ , show the maximum and minimum values.
- Explain why  $V_o$  is not a sinusoidal shape.



(1/5) Name \_\_\_\_\_ Student Number \_\_\_\_\_

(4/5) Please answer the following question in the space below:

The circuits below look similar, but give very different outputs ( $V_i$  is the input from another circuit).

- Briefly explain what each circuit does.
- Explain how they are different, and why.

