

**SYSC 3203**

**Project Title: EMG-Controlled Mouse**

**Laboratory: Deliverable #1B: Amplifier / gain stage**

1. Gain stage design

The gain stage should be a simple non-inverting op-amp design as shown in Figure 1.

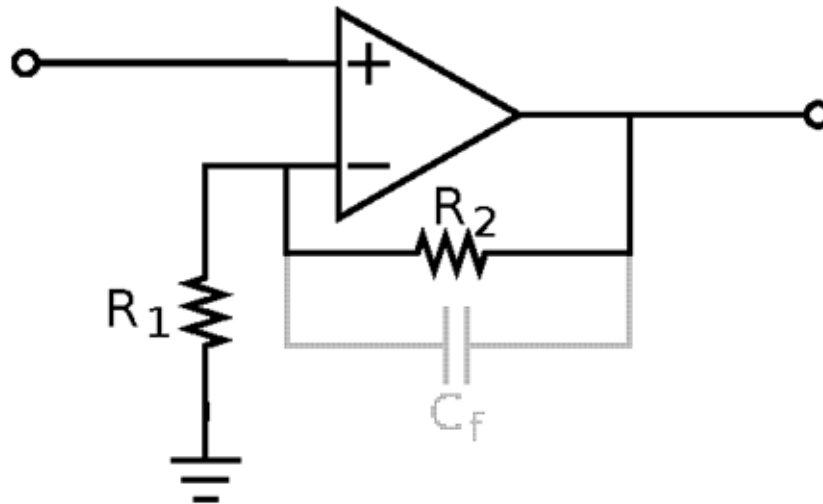


Figure 1: gain stage with optional low pass filtering

**1.1: Choose resistors  $R_1$  and  $R_2$  to give a voltage gain of x40. Show your calculations.**

**1.2: Choose  $C_f$  to make the gain of your circuit start to roll off above approximately 1 kHz. Show your calculations.**

2. Gain stage assembly and test

**2.1: Sketch the circuit diagram for the common-mode driver.**

**2.2: Draw a schematic of your circuit, showing the chip layout for the OP97 op-amp and labeling all of its terminals. Please also label the testing points for your circuit.**

Implement your gain stage using an OP97 op-amp from your kit. Using the function generator and oscilloscope:

**2.3: Verify that your circuit achieves the designed gain value. Explain your results to your TA.**

**2.4: Estimate the 3dB rolloff frequency of your circuit i.e. the frequency at which the output voltage reaches  $1/\sqrt{2}$  of its value at DC. Verify the result with your TA.**