

## SYSC 3203

### Project Title: EMG-Controlled Mouse

#### Lab Milestone #4A: Comparator and Trigger

In the previous lab, we obtained at the output of the integrator a signal indicating the intensity of the muscle contraction. The next step is to have a circuit that triggers for a given time whenever the intensity reaches a certain threshold. The goal for milestone #4 is to implement such a circuit by combining a comparator followed by a monostable circuit. In this lab you will implement the first part of this, consisting of a comparator followed by an edge trigger circuit.

## 1. Comparator

Design a comparator using the LT1011 voltage comparator that will compare the output of the integrator from the previous lab to an adjustable threshold (via a 10 k $\Omega$  potentiometer). The output of the comparator should be -3V or +3V.

**1.1: Sketch the circuit diagram for your voltage comparator.**

**1.2: Sketch a schematic of the chip layout for the LT1011 voltage comparator and labeling the terminals. Please label the testing points for your circuit.**

Build your comparator and test it using a function generator and an oscilloscope. You can use a sawtooth or triangular wave to show the comparator is working properly.

**1.3: Demonstrate your working comparator to your TA.**

## 2. Trigger circuit

The 555 monostable circuit that you will use in the next lab is a *negative edge triggered* device. In order to interface it to the comparator, a trigger circuit as represented in Figure 1 is required.

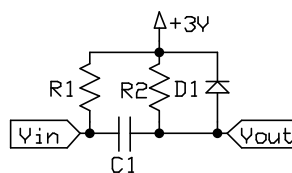


Figure 1: Trigger circuit

**2.1: Analyze the trigger circuit to figure out what it does. Draw the  $V_{out}$  signal if a square wave was present at the  $V_{in}$  input.**

**2.2: Select values for R1, R2, and C1 based on your desired time constant.**

**2.3: Sketch the circuit diagram for your trigger circuit, showing how it will connect to the voltage comparator.**

**2.4: Demonstrate your working trigger circuit to your TA.**