



The circuit above is exposed to the an input voltage V_i as shown. Sketch the output, V_o . At what times does $V_o = 100\text{ mV}$?
