



In the circuit above, V_1 is 1 V, and V_2 is 2 V.

- What is the value of V_o ?
 - How much current flows out of V_1 ?
-